

- 7 Fig. 7.1 shows an ideal transformer. The primary coil of the transformer has 4000 turns and is connected to a sinusoidal a.c. supply. The secondary coil has 200 turns and is connected to a $4.8\ \Omega$ load resistor and a diode.

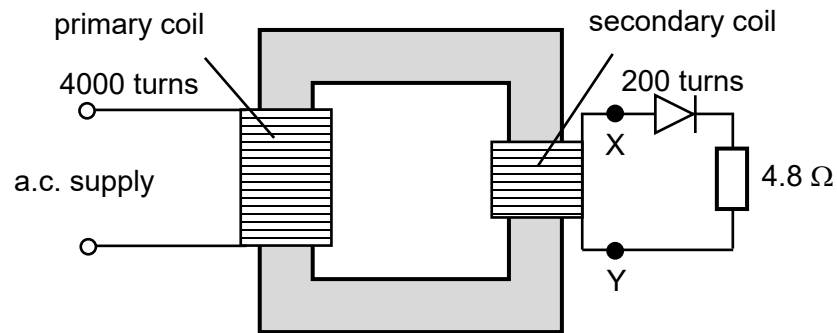


Fig. 7.1

V_{XY} is the potential of X with respect to Y. The variation with time t of V_{XY} is shown in Fig. 7.2.

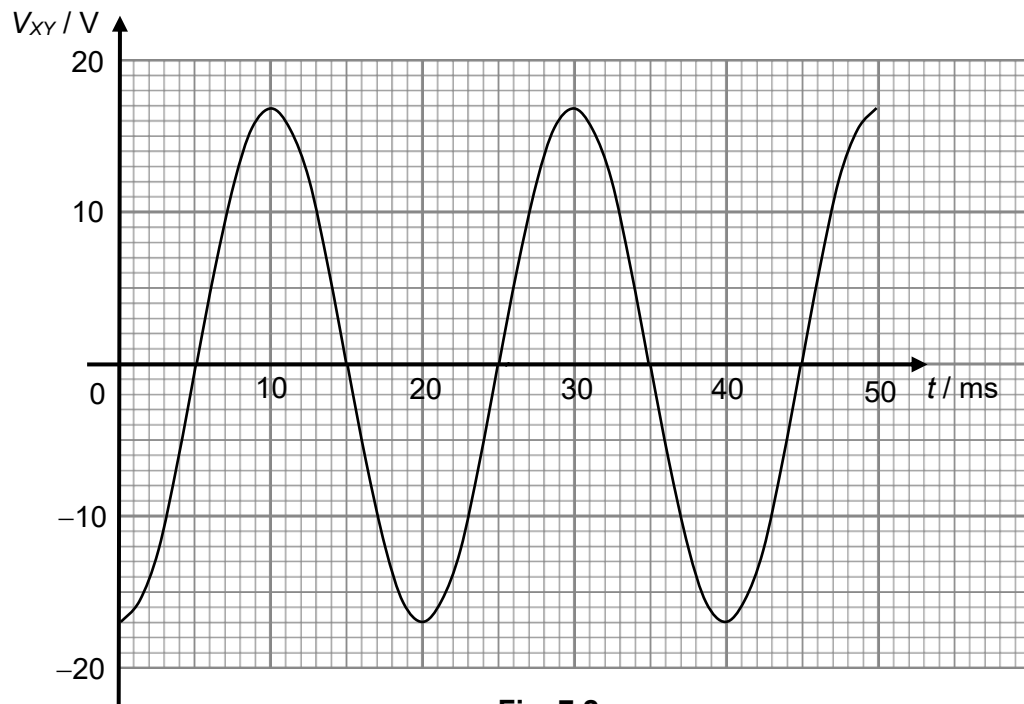


Fig. 7.2

(a) Determine the frequency of the a.c. supply.

frequency = Hz [1]

(b) Calculate the root-mean-square value of V_{XY} .

root-mean-square value of V_{XY} = V [1]

(c) Determine the root-mean-square voltage of the a.c. supply.

root-mean-square voltage = V [2]

(d) Determine the mean power dissipated in the load resistor.

mean power = W [2]

- (e) With reference to Fig. 7.2, describe and explain how the potential difference across the load resistor varies with time.

.....

.....

.....

[2]

.....

