

- 20** Two wires P and Q, of equal length and of same material, are connected in series to a battery. The diameter of P is half that of Q.

What is the ratio of $\frac{\text{current in P}}{\text{current in Q}}$?

A 0.25

B 0.5

C 1.0

D 4.0