

23

The current I through an electrical component is measured when a potential difference V is applied across it.

The graph shows the variation of I with V .

At which point is the resistance the greatest?

