

- 7 In a car, the power supply to two identical light bulbs R_1 and R_2 as shown in Fig. 7.1 consists of two power sources: a 12 V battery of internal resistance $0.20\ \Omega$ and a generator of 14 V connected in series with a variable resistor of resistance R . The resistance of each light bulb is $3.0\ \Omega$.

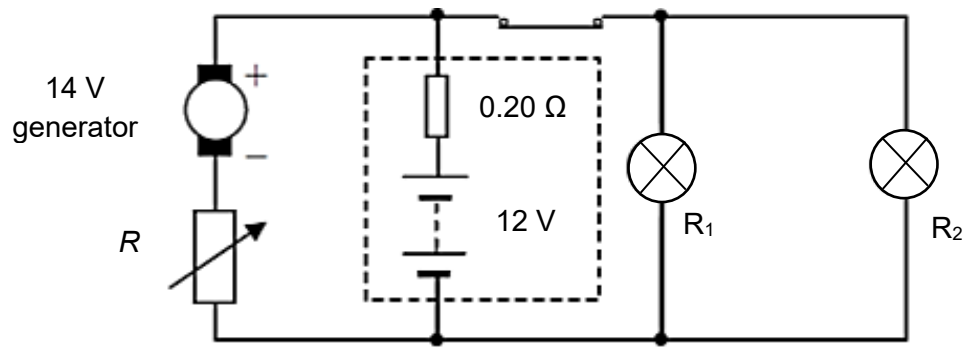


Fig. 7.1

- (a) Resistance R is adjusted so that there is no current in the 12 V battery when the light bulbs are turned on.

Show that $R = 0.25\ \Omega$. Explain your working.

- (b) A diode is connected to the circuit as shown in Fig. 7.2.

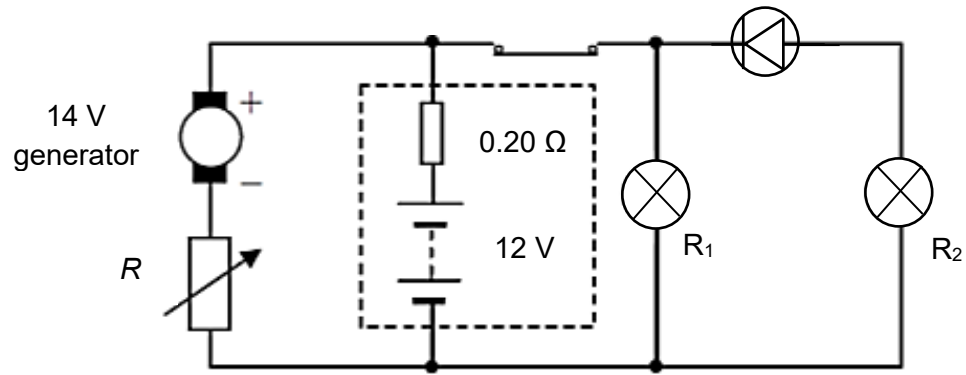


Fig. 7.2

Determine the value of R to maintain the current in the 12 V battery to be at zero ampere. Explain your working clearly.

$R = \dots\dots\dots \Omega$ [3]

- (c) Suggest two advantages which the circuit, as shown in Fig. 7.1, has over a single power source.

.....

..... [2]
...

