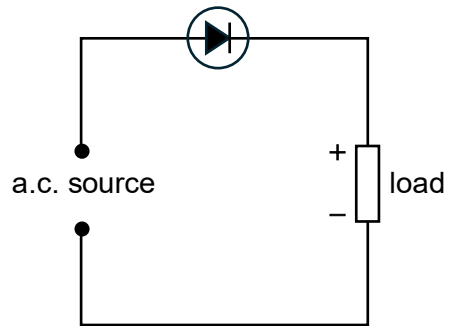



- 26** An a.c. source can be rectified to supply a d.c. to a load using a semiconductor diode, which is assumed to ideal.

Which of the following circuits will not correctly supply the required d.c. to the load?


A



B

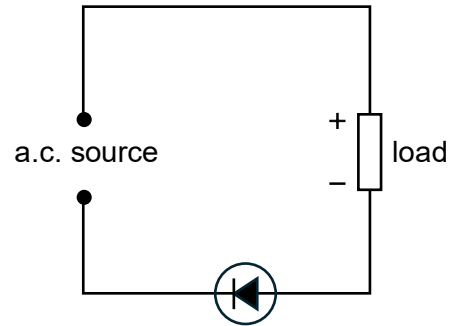

C

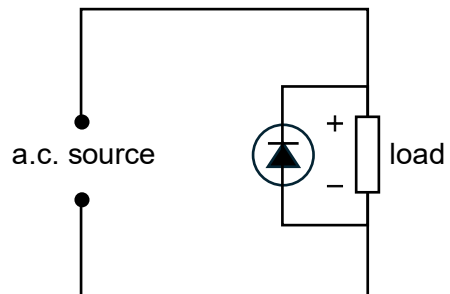

D

