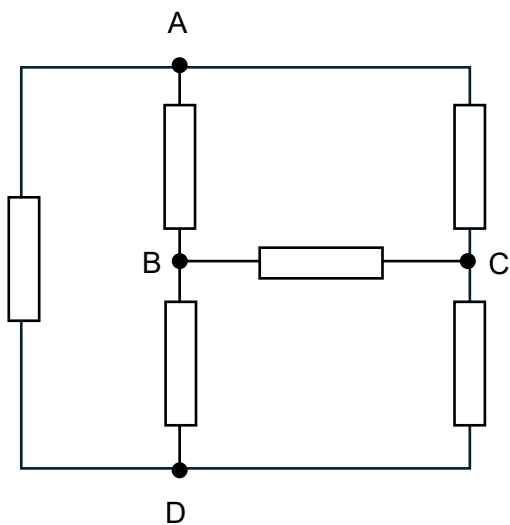


- 23** Six identical resistors are arranged in a circuit as shown below. Each resistor has a resistance of $6.0\ \Omega$.



What is the effective resistance between points A and D?

A $1.0\ \Omega$

B $2.0\ \Omega$

C $3.0\ \Omega$

D $6.0\ \Omega$

