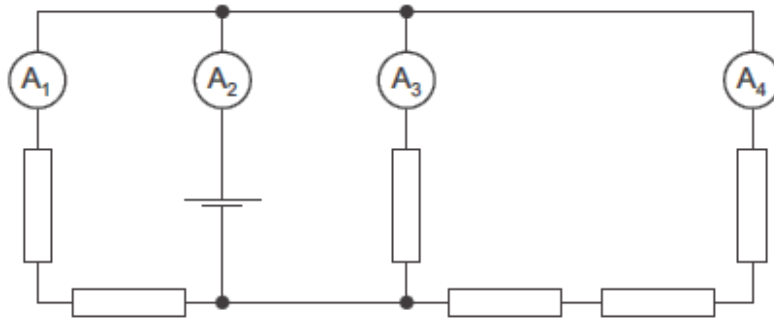


22

In the circuit shown, all the resistors are identical and the cell and all the ammeters have negligible resistance.



The reading of ammeter A_1 is 0.60 A.

What are the readings of the other ammeters?

	reading of ammeter A_2 / A	reading of ammeter A_3 / A	reading of ammeter A_4 / A
A	1.0	0.3	0.1
B	1.4	0.6	0.2
C	1.8	0.9	0.3
D	2.2	1.2	0.4