

- 5 A cell P, a fixed resistor R and a uniform resistance wire AB are connected in a circuit as shown in Fig. 5.1.

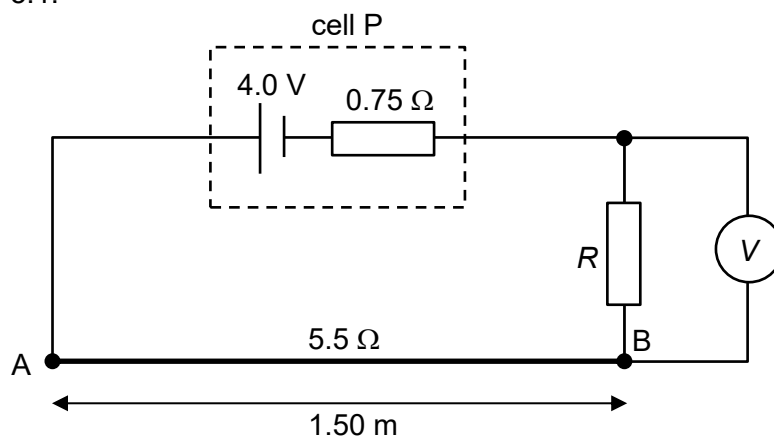


Fig. 5.1

Cell P has e.m.f. 4.0 V and internal resistance 0.75 Ω. Wire AB has length 1.50 m and resistance 5.5 Ω. The voltmeter reads 1.3 V.

- (a) Show that the potential difference across AB is 2.4 V. [2]

- (b) A cell Q and a sensitive ammeter are connected to the circuit in Fig. 5.1, as shown in Fig. 5.2.

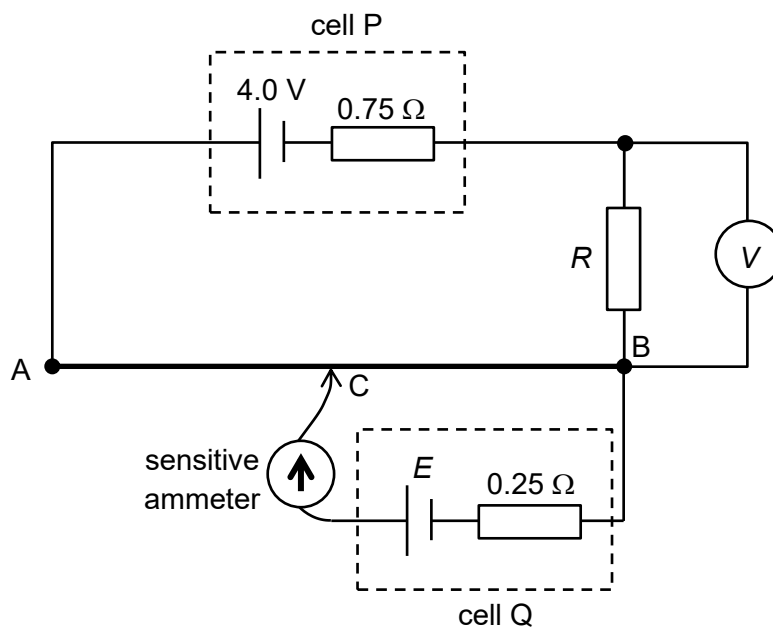


Fig. 5.2

Cell Q has e.m.f. E and internal resistance $0.25\ \Omega$. The ammeter reads zero when the length of AC is 0.56 m .

(i)

Determine E .

$$E = \dots\dots\dots \text{ V [2]}$$

(ii) There is a reading on the ammeter when the connection C is shifted closer to A.

State and explain the direction of the current across cell Q.

.....

.....

.....

.....

.....

[2]

- (d) The resistance wire AB is detached from the circuit and coiled in a circular manner as shown in Fig. 5.3. Metallic fasteners with negligible resistance are used to secure the wire at X and Y, where XY is the diameter of the coil.

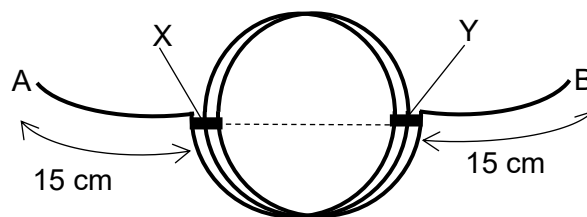


Fig. 5.3

- (i) Determine the resistance of wire AB when coiled in this manner.

resistance = Ω [3]

- (ii) An e.m.f. source is again connected across AB. State and explain whether the drift velocity of the electrons is greater in AX or in XY.

.....

.....

.....

.....

[2]

[Total: 11]