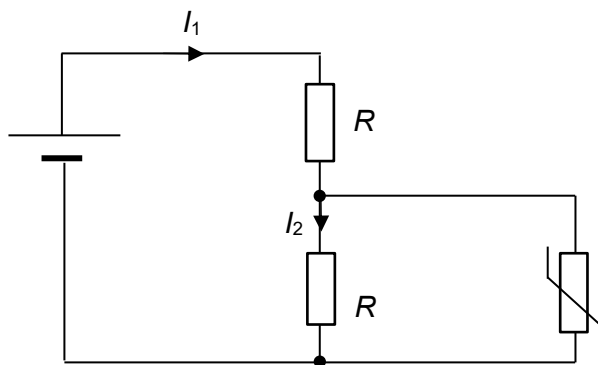


- 21 At room temperature, the resistance of a thermistor is R . It is connected to a circuit with two resistors, each of resistance R . The currents in the two resistors are I_1 and I_2 as shown.



How do the currents change when the temperature of the thermistor increases?

	I_1	I_2
A	increases	decreases
B	increases	increases
C	decreases	decreases
D	decreases	increases