

- 5 (a) The variation of an alternating voltage  $V_P$  in volts with time  $t$  in seconds is given by

$$V_P = 170 \sin (314t)$$

Determine

- (i) the r.m.s. potential difference  $V_{\text{r.m.s.}}$


$$V_{\text{r.m.s.}} = \dots\dots\dots \text{ V } [1]$$

- (ii) the period,  $T$  of the voltage supply.

$$T = \dots\dots\dots \text{ s } [1]$$

- (b) The alternating voltage  $V_P$  is connected to the primary coil of a transformer as shown in Fig. 5.1.

An electric heater with resistance  $130 \, \Omega$  is connected to the secondary coil of the transformer.

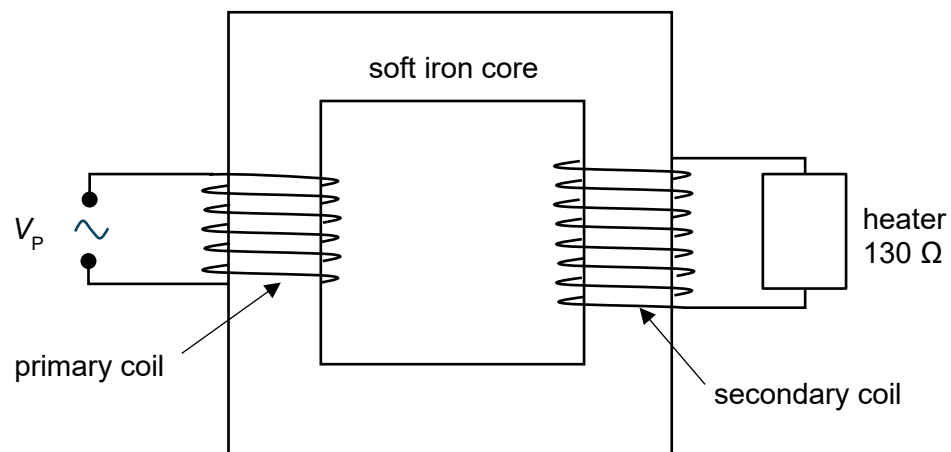

**Fig. 5.1**

The primary coil consists of 2000 turns and the secondary coil consists of 3500 turns.


- (i) Determine peak potential difference,  $V_s$  of the secondary coil.

$$V_s = \dots\dots\dots \text{ V } [2]$$

- (ii) Determine the peak current,  $I_p$  in the primary coil.

$$I_p = \dots\dots\dots \text{ A } [2]$$

- (c) A diode and another identical heater are connected to the secondary coil as shown in Fig. 5.2.

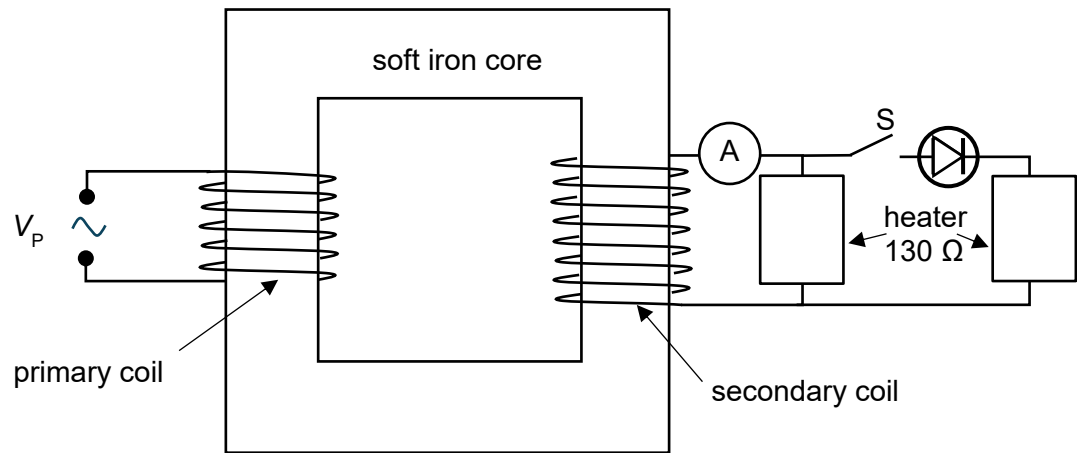

**Fig. 5.2**

Sketch on the axes of Fig. 5.3, the variation with time of the current  $I$  in the secondary coil when switch  $S$  is closed. Label the axes with appropriate values. Include on your graph a time equal to two periods of the alternating potential difference.



**Fig. 5.3**