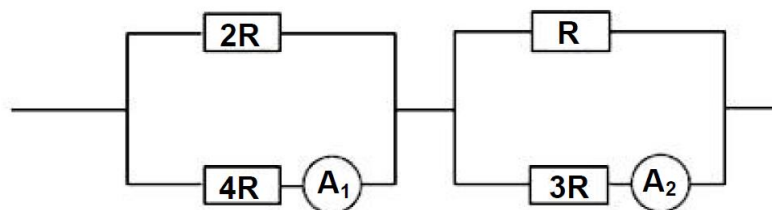


- 22 The circuit shown in the diagram below is connected to a power supply.



If ammeter A_1 reads 6.0 A , what is the reading on ammeter A_2 ?

- A** 13.5 A **B** 6.0 A **C** 4.5 A **D** 2.3 A

