

- 6 (a) A uniform wire AB of length 150 cm and radius 0.45 mm is connected in series with a cell E of e.m.f. 6.0 V with negligible internal resistance as shown in Fig. 6.1.

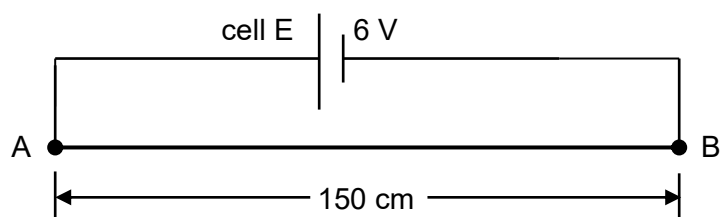


Fig. 6.1

The resistivity of the wire is $1.1 \times 10^{-6} \, \Omega \text{ m}$.

Determine the resistance of the wire.

[2]

resistance = Ω

- (b) A cell C of e.m.f. 1.5 V with internal resistance r is connected to the circuit of Fig. 6.1, as shown in Fig. 6.2.

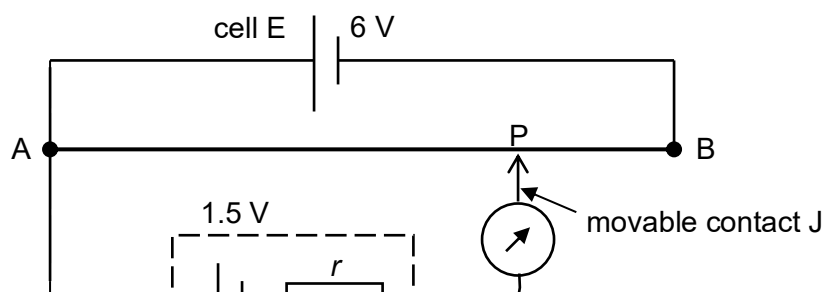


Fig. 6.2

The movable contact J can be connected to any point along the wire AB.

- (i) Determine the length AP required to produce zero current in the galvanometer.

[2]

length AP = m

- (ii) An additional resistor, R , of resistance $2.0\ \Omega$ is now connected between the terminals of cell C as shown in Fig. 6.3, and it produces a balance length of 25 cm from A.

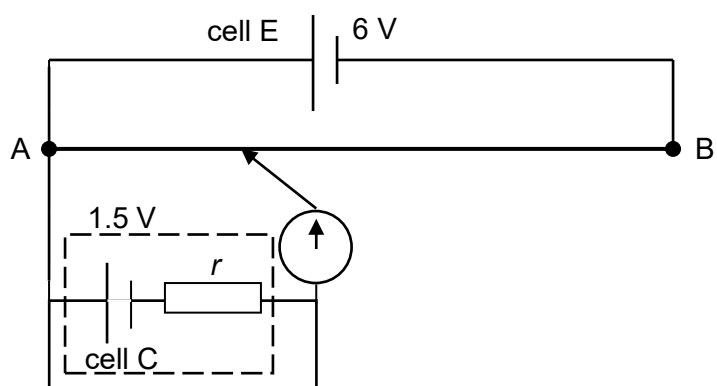


Fig. 6.3

Determine the internal resistance of cell C.

[3]

internal resistance = Ω

- (iii) After prolonged use, the internal resistance of cell E may increase and become significant.

State and explain how the balance length mentioned in part **(b)(ii)** will change.

.....

.....

[2]

.....

.....