

- 6 (a) A simple iron-cored transformer is illustrated in Fig. 5.1.

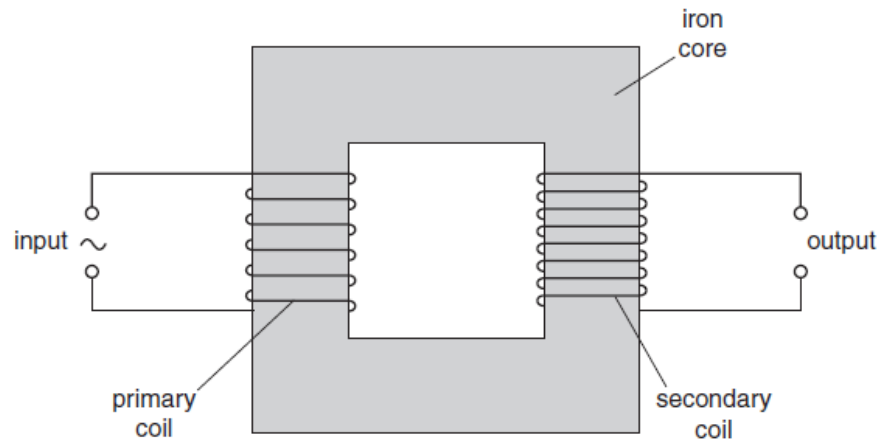


Fig. 5.1

- (i) Explain why the primary and secondary coils are wound on a core made of iron.

.....
..... [1]

- (ii) Suggest why thermal energy is generated in the core when the transformer is in use.

.....
.....
.....
.....
.....
..... [2]

- (b) A student is asked to design a circuit by which a direct voltage of peak value 9.0 V is obtained across a load from a 240 V alternating supply. The student uses a transformer that may be considered to be ideal and a rectifier incorporating an ideal diode.

The partially completed circuit diagram is shown in Fig. 5.2.

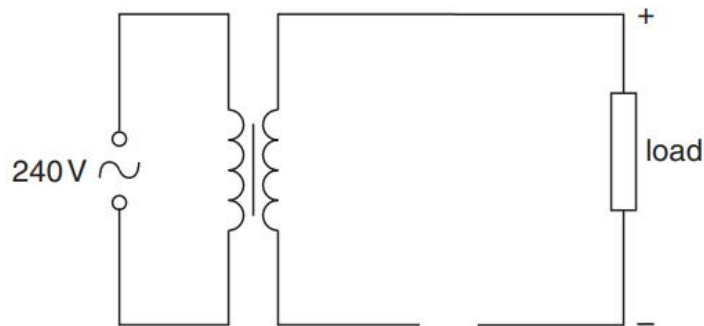


Fig. 5.2

- (i) On Fig. 5.2, insert a symbol for the diode so as to produce the polarity across the load as shown on the diagram. [1]

- (ii) Calculate the ratio

$$\frac{\text{number of turns in the secondary coil}}{\text{number of turns in the primary coil}}.$$

ratio =

[3]

- (iii) The load has a resistance of 4.5 Ω .

Calculate the mean power dissipated in the load.

mean power = W [2]
[Total: 9]

Section B

Answer **one** question from this Section in the spaces provided.