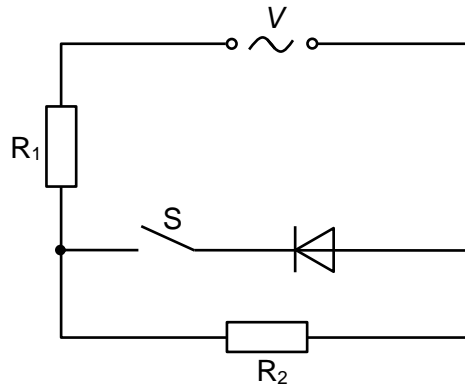


- 6 (a) By reference to heating effect, state what is meant by the *root-mean-square* value of an alternating current.

.....  
.....  
..... [1]

- (b) An alternating power supply is connected to a switch S, an ideal diode and two identical resistors  $R_1$  and  $R_2$ , as shown in Fig. 6.1. Each resistor has a resistance of  $18\ \Omega$ .



**Fig. 6.1**

The variation with time  $t$  of the potential difference  $V$  of the alternating supply is given by the expression

$$V = 24 \sin 314 t$$

where  $V$  is in volts and  $t$  is in seconds.

- (i) Switch S is closed.

On Fig. 6.2, show the variation with time  $t$  of the potential difference  $V_1$  across  $R_1$  for two periods of the alternating voltage.

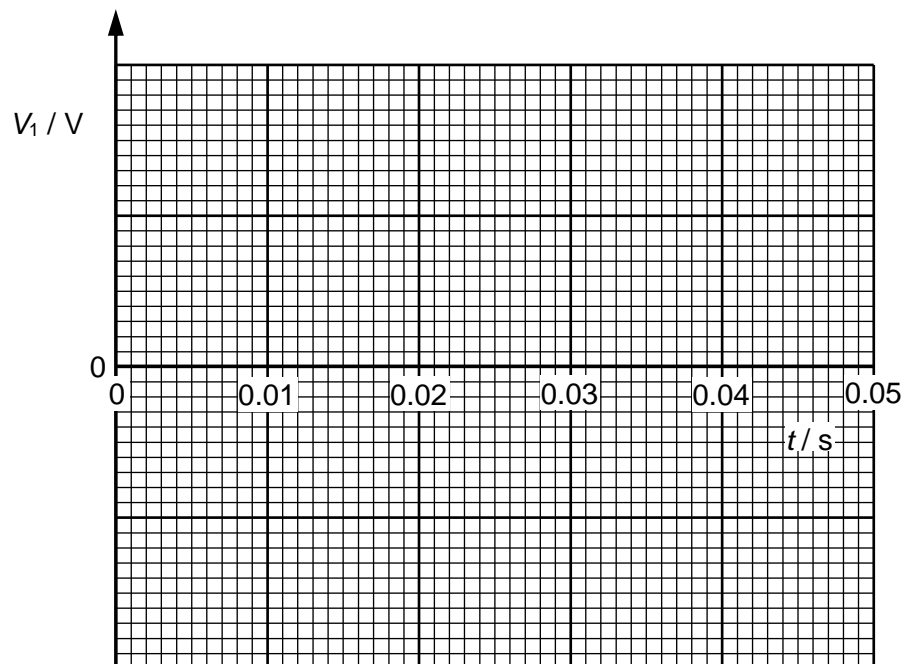


Fig. 6.2

[2]

- (ii) Switch S is opened.

On Fig. 6.3, draw the variation with time  $t$  of the power  $P_1$  transferred in  $R_1$  for two periods of the alternating voltage.

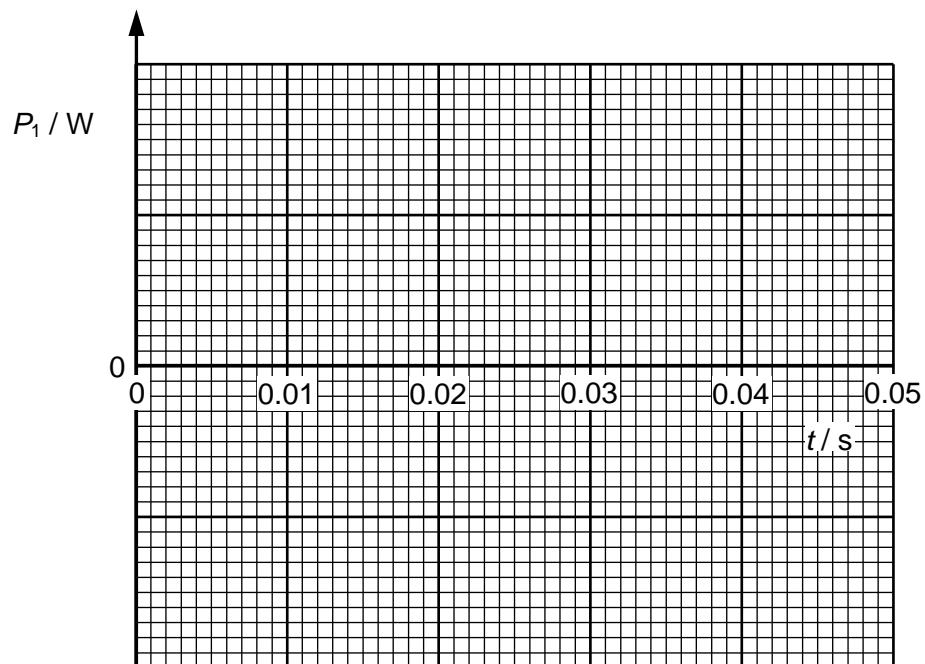


Fig. 6.3

[2]