

- 3 An alternating supply of frequency 50 Hz and having an output of 6.0 V r.m.s. is to be rectified so as to provide direct current for a resistor R. The circuit of Fig. 3.1 is used.

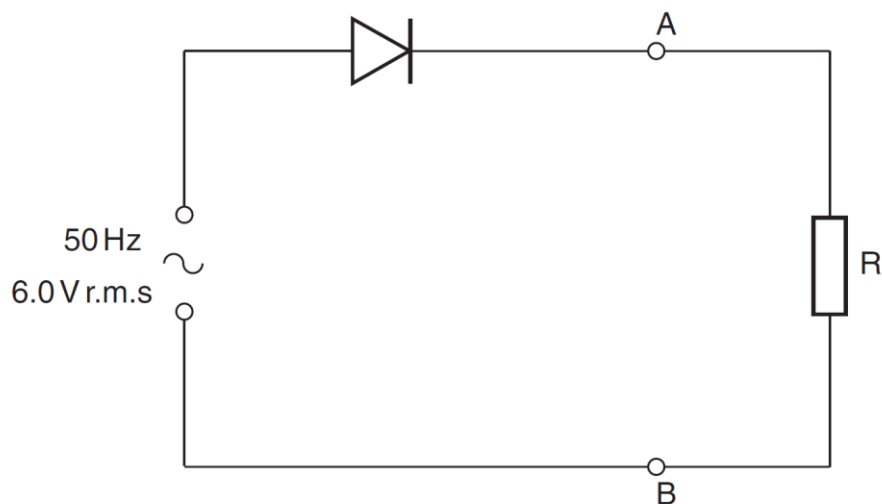


Fig. 3.1

The diode is ideal.

The output potential difference V of the alternating power supply is represented by

$$V = V_o \sin(kt)$$

where V_o is the maximum potential difference in volts and t is the time in seconds.

- (a) By reference to heating effect, state what is meant by the *root-mean-square (r.m.s.)* of an alternating current.

.....

[1]

- (b) Determine the value of V_o

$V_o = \dots\dots\dots$ V [1]

- (c) Determine the value and unit of k .

value of k = unit [2]

- (d) Determine the maximum potential difference across the diode during one cycle.

potential difference = V [1]


- (e) State the potential difference across A and B when the diode has maximum potential difference across it. Give a reason for your answer.

.....
 [1]

- (f) R has a resistance of $5.0 \, \Omega$.

In Fig. 3.2, sketch the variation with time of the power dissipated in R for **one** period of the alternating supply.

power

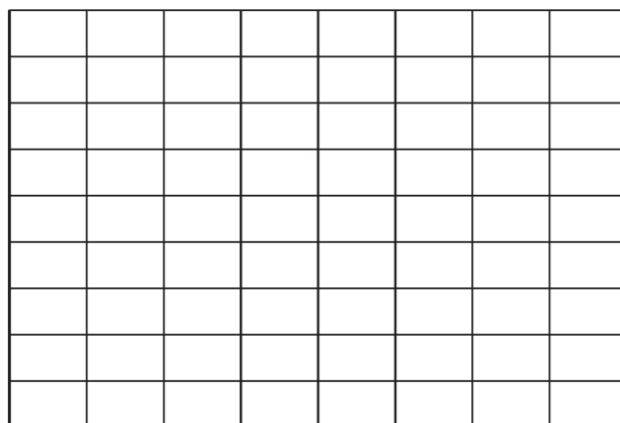

time

Fig. 3.2

