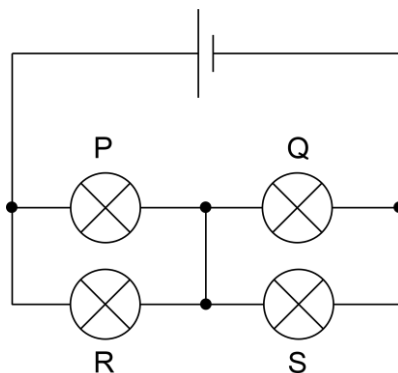


23 A cell is connected to four identical lamps as shown.



What happens when lamp Q is blown out?

- A** Lamp P becomes brighter than before.
- B** Lamp S becomes brighter than before.
- C** Lamp S does not light up.
- D** Lamps P and R remain as bright as before.

[Turn over]