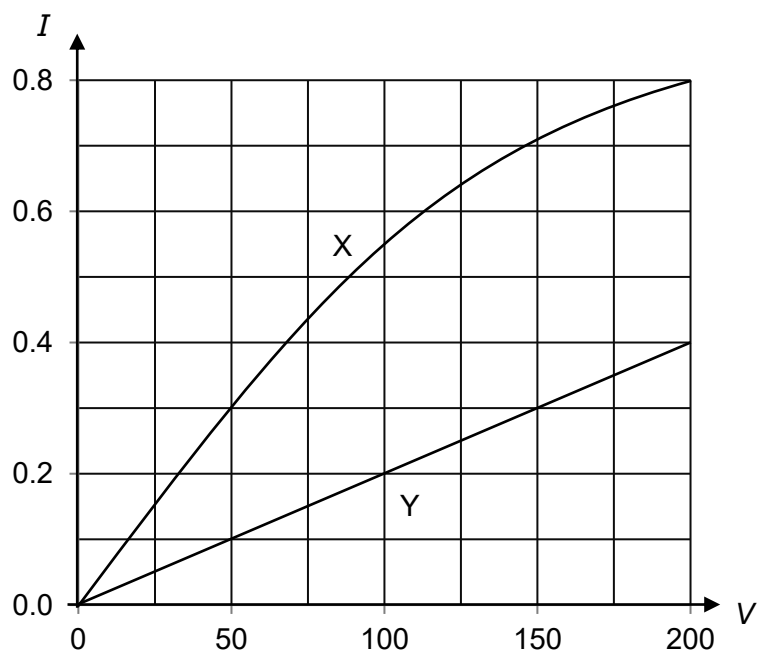


- 22** The graph below shows the I - V graph of two electrical components X and Y. X and Y are connected in series to a 200 V supply.



What is the power dissipated in each component?

	power dissipated in X / W	power dissipated in Y / W
A	13	38
B	15	45
C	55	20
D	160	80

