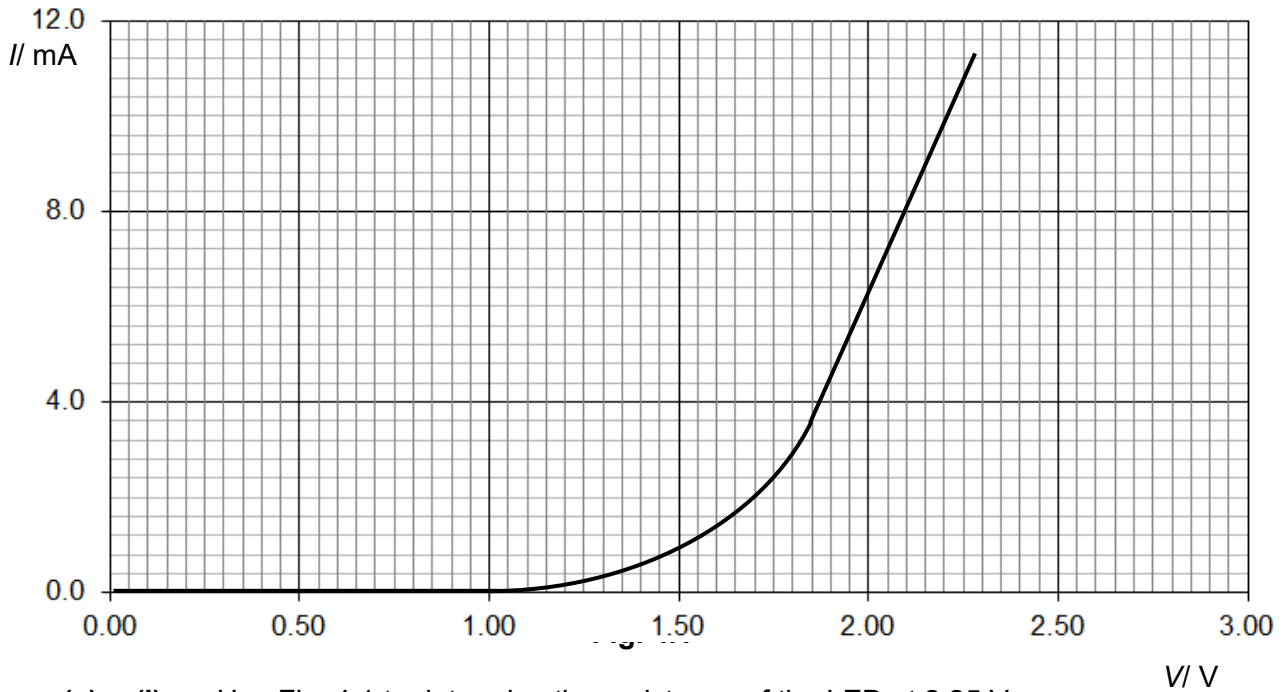


[1]

- 4 The variation with potential difference V of current I for a light emitting diode (LED) is shown in Fig. 4.1.



- (a) (i) Use Fig. 4.1 to determine the resistance of the LED at 2.25 V.

resistance = Ω [1]

- (ii) Shade in Fig. 4.1 the area that represent the increase in power dissipation in the LED if the potential difference across the LED is increased from 1.50 V to 1.75 V.

[1]

- (b) Two of these LEDs are connected to a 3.0 V battery with negligible internal resistance and a 160 Ω resistor as shown in Fig. 4.2.

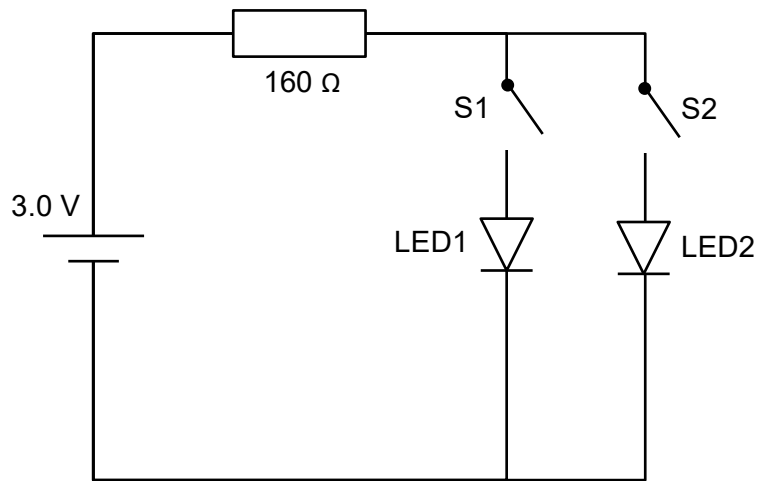


Fig. 4.2

- (i) Draw in Fig. 4.1 the variation with potential difference of current for the $160\ \Omega$ resistor. Label the line **R** [1]
- (ii) Hence, or otherwise, determine the current in LED1 when switch S1 is closed and switch S2 remaining open. Show your working clearly.

current = mA [2]

- (iii) Explain why LED1 becomes dimmer when S2 is also closed.

.....

.....

.....

.....

..... [3]

- (c) It is possible for LED1 to have the same brightness regardless of whether S2 is open or closed with the addition of another $160\ \Omega$ resistor and rearrangement of the circuit in Fig. 4.2.

Draw this circuit in the space below.

[1]