

- 22** In bright light, a light-dependent resistor (LDR) has a resistance of R . It is connected in series with an ideal diode and a fixed resistor of resistance R . An ideal diode has zero resistance in the forward direction and infinite resistance in the reverse direction.

In which arrangement will the potential at **X** increase when the circuit is moved to a darker environment?

