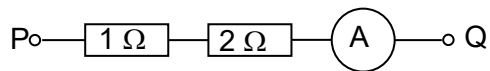



23

In which of the following circuits will the ammeter A of  $2.0\ \Omega$  give the largest reading? The potential difference across PQ has the same value for each of the circuits shown.


A



B

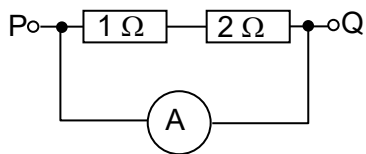

C

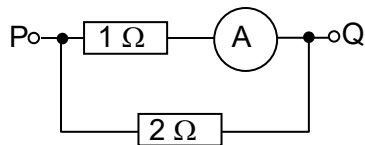

D

