

- 25** When a varying voltage is connected across a resistor of resistance $8.0\ \Omega$, the mean power dissipated in the resistor is $450\ \text{W}$.

Which graph shows a possible variation of the voltage with time?

