

- 5 (a) Three bulbs X, Y and Z are connected to a cell as shown in Fig. 5.1.

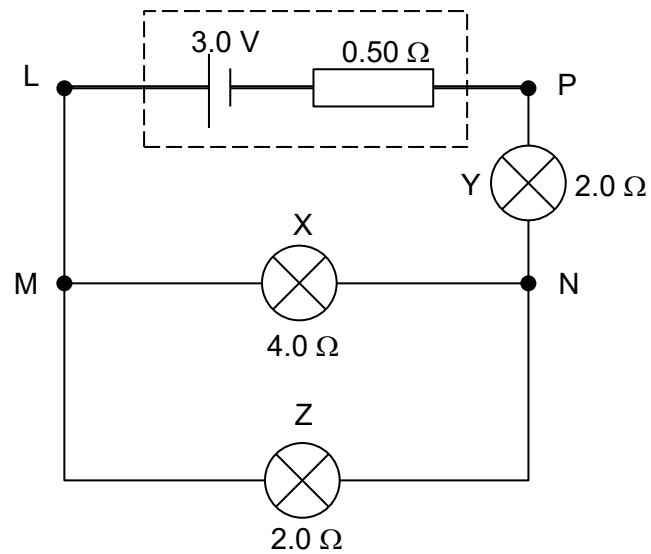


Fig. 5.1

The cell has an e.m.f. 3.0 V and internal resistance 0.50 Ω .

- (i) Determine the terminal potential difference across LP.

terminal potential difference = V [2]

- (ii) List the three light bulbs in order of increasing brightness.

increasing order:,, [1]

- (b) The circuit in Fig. 5.1 was connected to a potentiometer consisting of a 6.0 V battery in series with a resistor of resistance $R = 1.0\ \Omega$, and a uniform wire AB of length 100.0 cm and resistance $2.0\ \Omega$, as shown in Fig. 5.2.

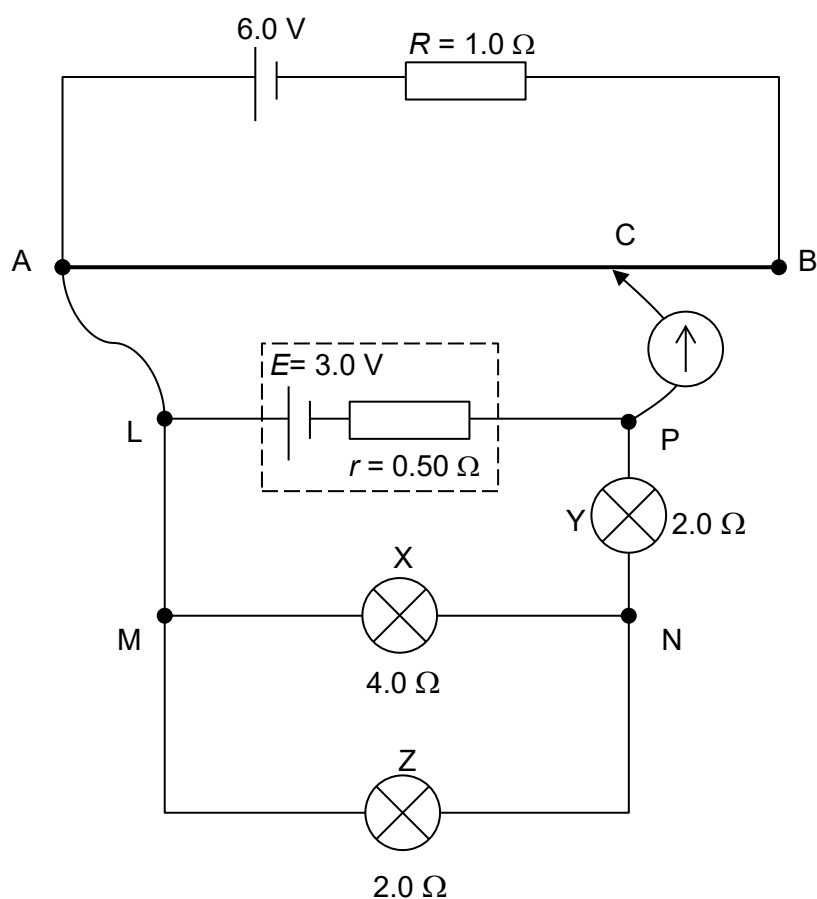


Fig. 5.2

- (i) Determine the potential difference across AB.

potential difference = V [1]

(ii) Determine the balance length AC.

length AC = cm [2]

(iii) Explain how the balance length AC will be affected if bulb X is replaced by a bulb which has a lower resistance.

.....
.....
.....
..... [2]