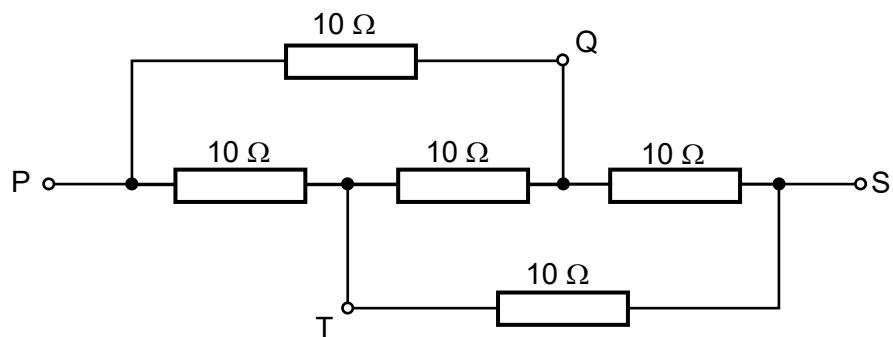


**22** A network of resistors each of resistance  $10\ \Omega$  are shown.



What is the effective resistance between Q and T?

- A**  $2.0\ \Omega$
- B**  $5.0\ \Omega$
- C**  $10\ \Omega$
- D**  $12\ \Omega$