

- 24** An alternating potential difference $V = V_0 \sin(\omega t)$ is applied across a resistor in a circuit, causing a current $I = I_0 \sin \omega t$ to flow in the resistor. The mean power dissipated in the resistor is

A $V_0 I_0 \sqrt{2}$

B $\frac{V_0 I_0}{2}$

C $\frac{V_0 I_0}{\sqrt{2}}$

D zero