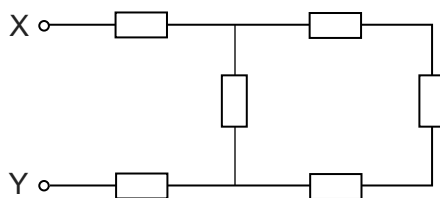


- 19 6 identical resistors of resistance R are set up across points X and Y as shown in the diagram below. What is the effective resistance across X and Y in terms of R ?



- A $1.50 R$
- B $2.75 R$
- C $3.33 R$
- D $5.00 R$

