

- 5 A battery of electromotive force (e.m.f.) 12 V and negligible internal resistance is connected to a network of two lamps and two resistors, as shown in Fig. 5.1.

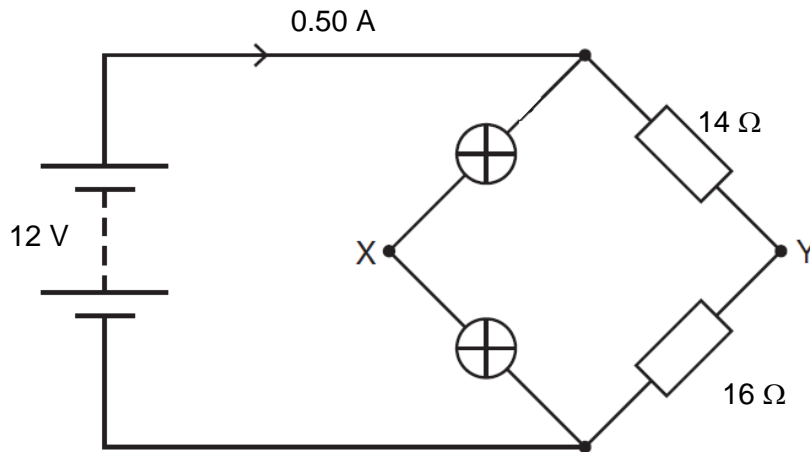


Fig. 5.1

The two lamps in the circuit have equal resistances. The two resistors have resistances $14\ \Omega$ and $16\ \Omega$. The lamps are connected at junction X and the resistors are connected at junction Y. The current in the battery is $0.50\ \text{A}$.

- (a) The two filament lamps are observed to take a few seconds to achieve their full brightness. Explain why this is so.

.....

[2]

- (b) Calculate the potential difference across the $16\ \Omega$ resistor.

potential difference =V [2]

- (c) (i) Determine the potential difference between points X and Y.

potential difference =V [1]

- (ii) State whether point X or point Y is at a higher potential.

.....[1]

- (d) Show that the current in the lamps is 0.10 A.

[1]

- (e) Calculate the ratio

$$\frac{\text{total power dissipated by the lamps}}{\text{total power produced by battery}}$$

ratio =[2]

- (f) The $14\ \Omega$ is replaced by another resistor of higher resistance.

State and explain the effect, if any, of this change on the ratio in (e).

.....

 [2]

[Total: 11]