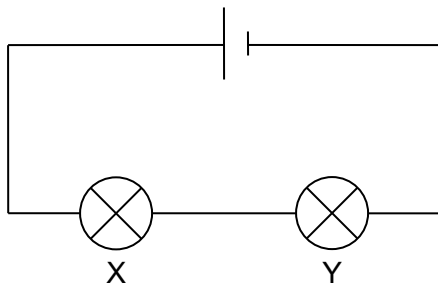


- 22 The circuit below contains a cell and 2 identical lamps X and Y. What will happen to the brightness of the 2 lamps if an additional identical lamp is added in parallel to X?



- A Both X and Y are less bright.
- B X is less bright, Y is brighter.
- C X is brighter, Y is less bright.
- D Both X and Y are brighter.