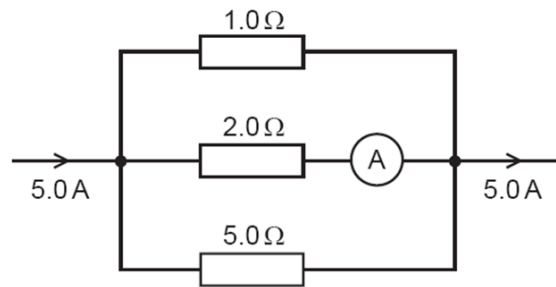


- 22** The diagram shows part of a current-carrying circuit. The ammeter has negligible resistance.



What is the reading on the ammeter?

- A** 0.70 A                      **B** 1.3 A                      **C** 1.5 A  
**D** 1.7 A