
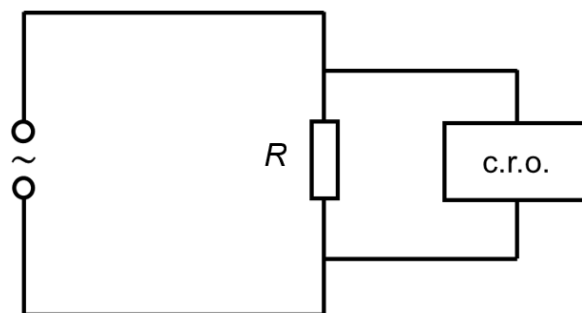


- 6 An a.c. power supply is connected to a resistor  $R$ , as shown in Fig. 6.1.

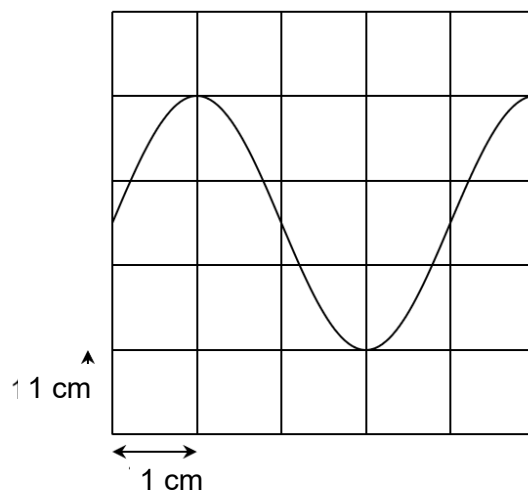

**Fig. 6.1**

A cathode ray oscilloscope (c.r.o.) is used to show the potential difference (p.d.) across  $R$ . The screen of the c.r.o. displays the variation with time of the p.d. across  $R$ , as shown in Fig. 6.2.



**Fig. 6.2**

- (a) Explain, by reference to direct current, what is meant by the *root-mean-square* (r.m.s.) value of an alternating current.

.....  
 .....  
 .....  
 .....  
 .....  
 [2]

- (b) The voltage  $V$  of the power supply is given by the expression

$$V = 6.0 \sin(100\pi t)$$


$V$  is measured in volts and the time  $t$  is measured in seconds.

Determine the Y-gain and time-base of the c.r.o.

Y-gain = ..... V / cm


time-base = ..... ms / cm  
[2]

(c) A diode is then connected in series with the resistor  $R$ , as shown in Fig. 6.3.

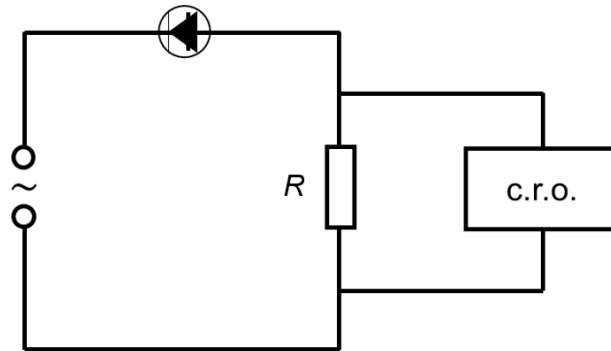

**Fig. 6.3**

- (i) Sketch in Fig. 6.4, for 2 periods of the alternating p.d., the variation with time of the power  $P$  dissipated in  $R$  when  $R$  is  $20\ \Omega$ , where  $T$  is the period. Indicate the peak power value in your sketch. [2]

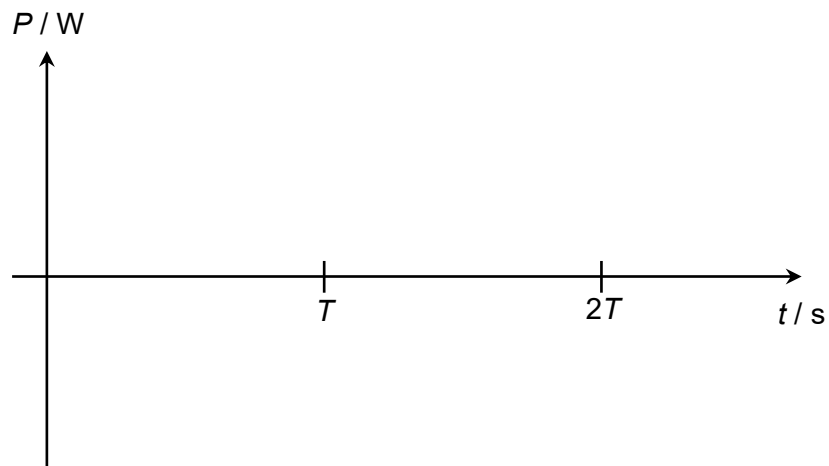

**Fig. 6.4**

- (ii) Draw a line in Fig. 6.4 to represent the average power dissipated in  $R$ . Indicate its value on the y-axis. [1]
- (iii) Calculate the root-mean-square current in  $R$ .

root-mean-square current = ..... A [2]

[Total: 9]



