
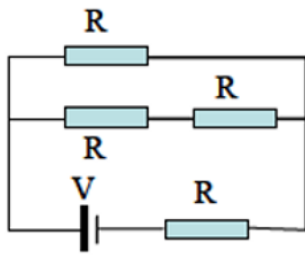


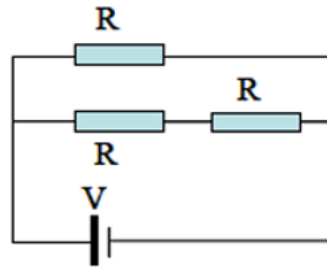
- 15 Four circuits are shown below. The batteries all have the same voltage V and all resistors have the same resistance R . In which circuit does the battery produce the most power?




A



B

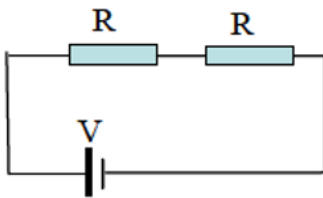

C

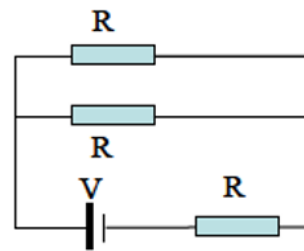

D