

- 5 Fig. 5.1 shows a circuit that consists of a lamp, an ammeter, a voltmeter and a battery of unknown electromotive force (e.m.f.).

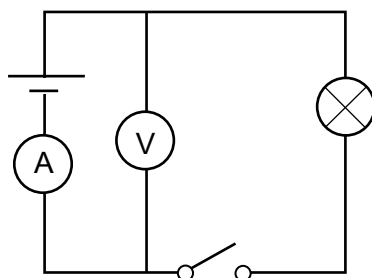


Fig. 5.1

When the switch is open, the ammeter and the voltmeter read 0 A and 3.00 V, respectively. When the switch is closed, the meters read 1.60 A and 2.20 V.

- (a) State the e.m.f. of the battery.

e.m.f. = \_\_\_\_\_ V [1]  
.....

- (b) Determine the internal resistance of the battery.

internal resistance = \_\_\_\_\_  $\Omega$  [2]  
.....

(c) (i) Calculate the power delivered to the lamp.

power = ..... W [1]

(ii) Determine the efficiency of the power transfer of the battery.

efficiency = ..... % [2]