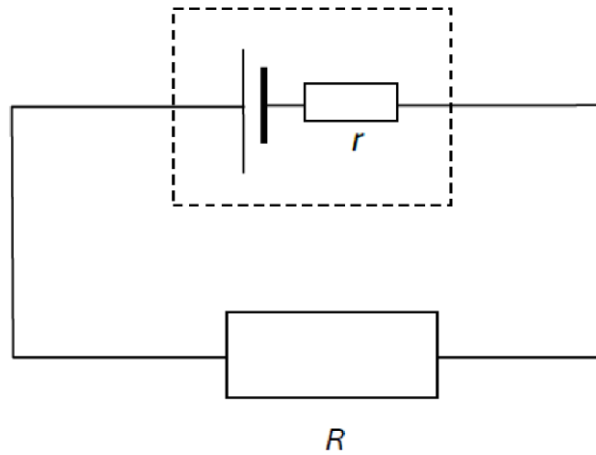


- 22** A battery with internal resistance r is connected to a resistor R as shown in the figure below. A constant current passes through R . When a charge of 20.0 C passes through the circuit, the heat dissipated in r is 10.0 J and the heat dissipated in R is 50.0 J.



What is the e.m.f. of the battery and the potential differences across r and R ?

	e.m.f. of the battery	potential difference across r	potential difference across R
A	6.00 V	1.00 V	5.00 V
B	6.00 V	5.00 V	1.00 V
C	3.00 V	2.50 V	0.50 V
D	3.00 V	0.50 V	2.50 V