

6

(a)


A student wishes to determine the I - V characteristics of a semiconductor diode.



(i)

Draw a suitable labelled diagram of the circuit that would enable the student to collect data to determine the I - V characteristics of the semiconductor diode.

[2]

 


(ii)

Sketch, on Fig. 6.1, the I - V characteristics of a semiconductor diode in forward bias.



Fig. 6.1

[1]

 


(iii)

State how the resistance of the diode can be determined from Fig. 6.1.

.....

..... [1]

 

(b)

Four ideal diodes are arranged in the circuit as shown in Fig. 6.2.

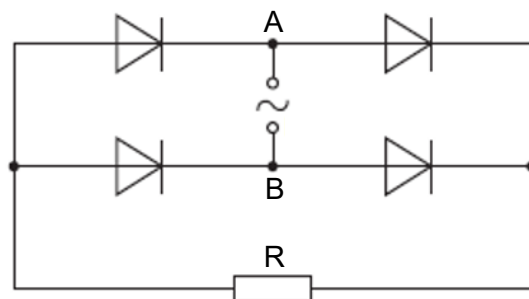


Fig. 6.2

A 7.0 V sinusoidal a.c. voltage supply at 25 Hz is applied between points A and B.


(i)

Circle the diode(s) that conduct when point B is positive with respect to point A. [1]

(ii)

Calculate the maximum voltage V_{\max} across the resistor R.

$V_{\max} = \dots\dots\dots$ V [1]

 

(iii)

Three of the diodes are removed and resistor R is connected to a diode, a cathode-ray oscilloscope (c.r.o.) and the 7.0 V sinusoidally-alternating voltage supply via a switch as shown in Fig. 6.3.

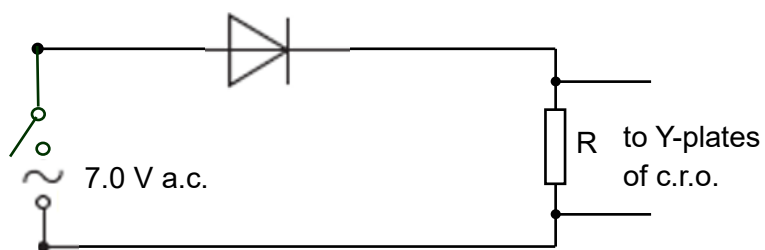


Fig. 6.3

The Y-plate sensitivity of the c.r.o is 5.0 V cm^{-1} and time base is 10 ms cm^{-1} .

When the switch is opened, a horizontal trace is obtained as shown in Fig. 6.4.

Fig. 6.4



1.

Sketch, on Fig. 6.4, the full trace shown on the c.r.o. screen when the switch is closed.
[2]



2.

Calculate the resistance of resistor R given that the mean power dissipated in it is 4.5 W.

resistance = Ω [2]

[Total: 10]