

- 4 (a) Distinguish between electromotive force (e.m.f.) and potential difference (p.d.).

.....  
.....  
..... [1]

- (b) A battery of e.m.f.  $E_1$  and internal resistance  $r_1$  is connected in series with a variable resistor  $R$  as shown in Fig. 4.1.


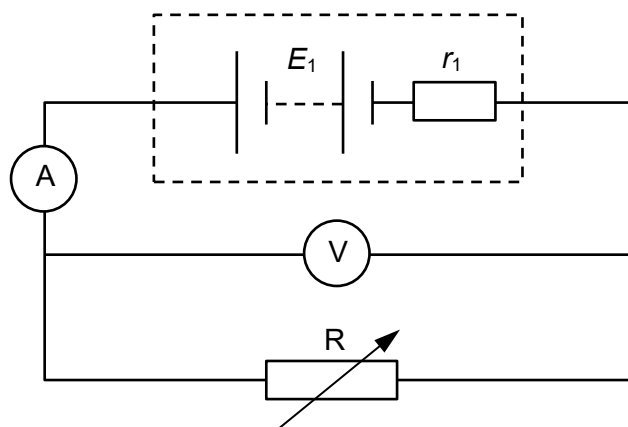


Fig. 4.1

Readings from the ammeter and the voltmeter are taken as the resistance of  $R$  is varied. Fig. 4.2 shows the variation with the voltmeter reading  $V$  of the ammeter reading  $I$ .

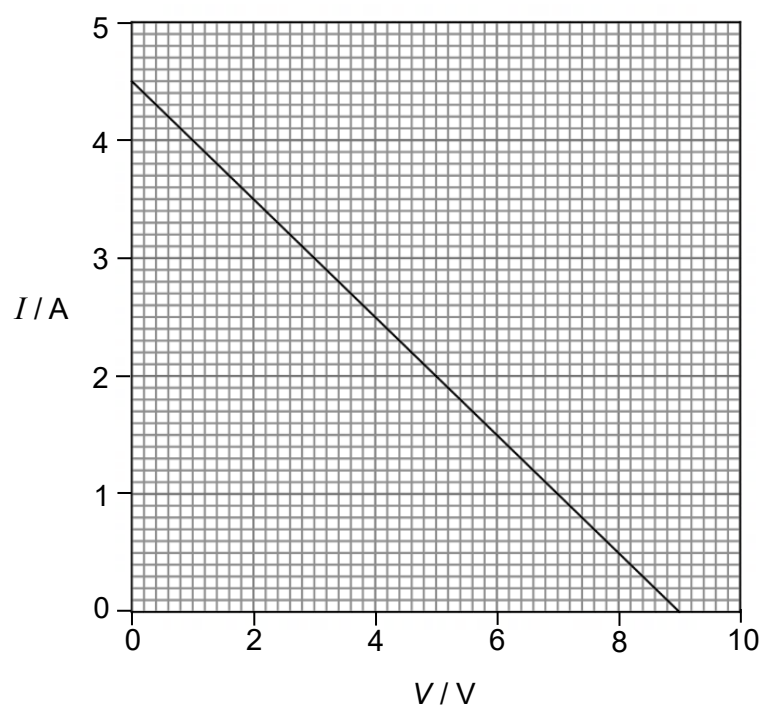

**Fig. 4.2**

Use Fig 4.2 to determine for the battery,

- (i) its e.m.f.  $E_1$ ,


$$E_1 = \dots\dots\dots \text{V} \quad [1]$$

- (ii) its internal resistance  $r_1$ .

$$r_1 = \dots\dots\dots \Omega \quad [2]$$

- (c) The ammeter and voltmeter are removed and the variable resistor R is set at  $4.0 \Omega$ .

A uniform resistance wire XY, a cell C, a switch S, a  $5.0 \Omega$  resistor and a galvanometer are connected to the circuit of Fig 4.1, as shown in Fig 4.3. J is a movable electrical connection.

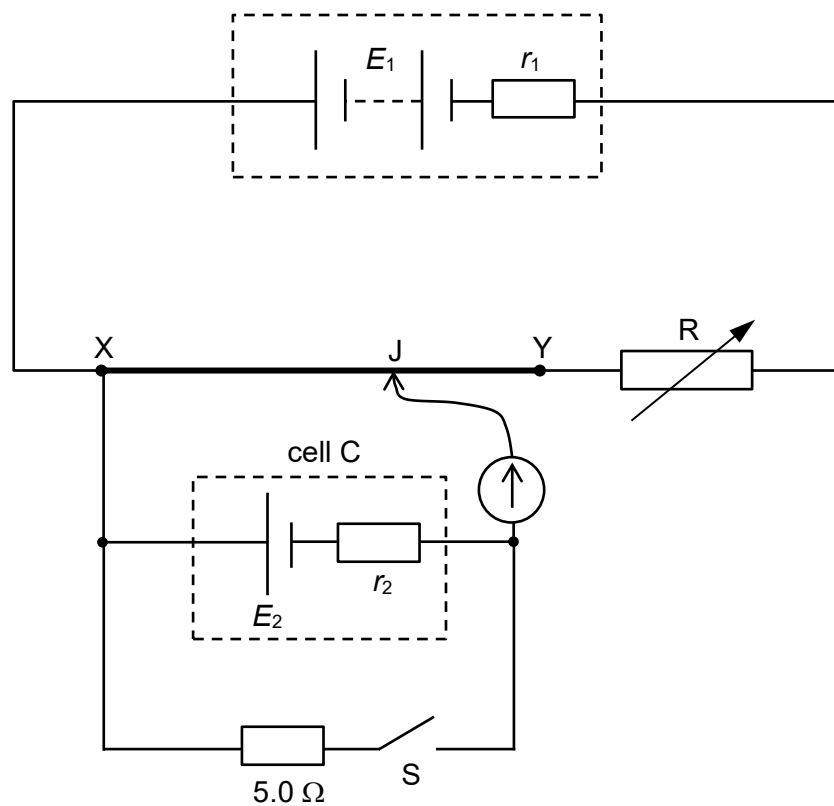

**Fig 4.3**

The wire XY has length 1.0 m and resistance  $4.0\ \Omega$ . Cell C has an e.m.f.  $E_2$  and internal resistance  $r_2$ .

With switch S opened, the galvanometer shows null deflection when XJ is 0.75 m.  
With switch S closed, the galvanometer shows null deflection when XJ is 0.30 m.

(i) Calculate for Cell C,


1. its e.m.f.  $E_2$ ,

$E_2 = \dots\dots\dots$  V [2]

2. its internal resistance  $r_2$ .

$r_2 \dots\dots\dots$   $\Omega$  [2]

- (ii) Another uniform resistance wire PQ is connected across XY as shown in Fig. 4.4. The wire PQ has length 1.0 m and resistance  $8.0\ \Omega$ . With switch S opened, a new balance length XJ' is found.

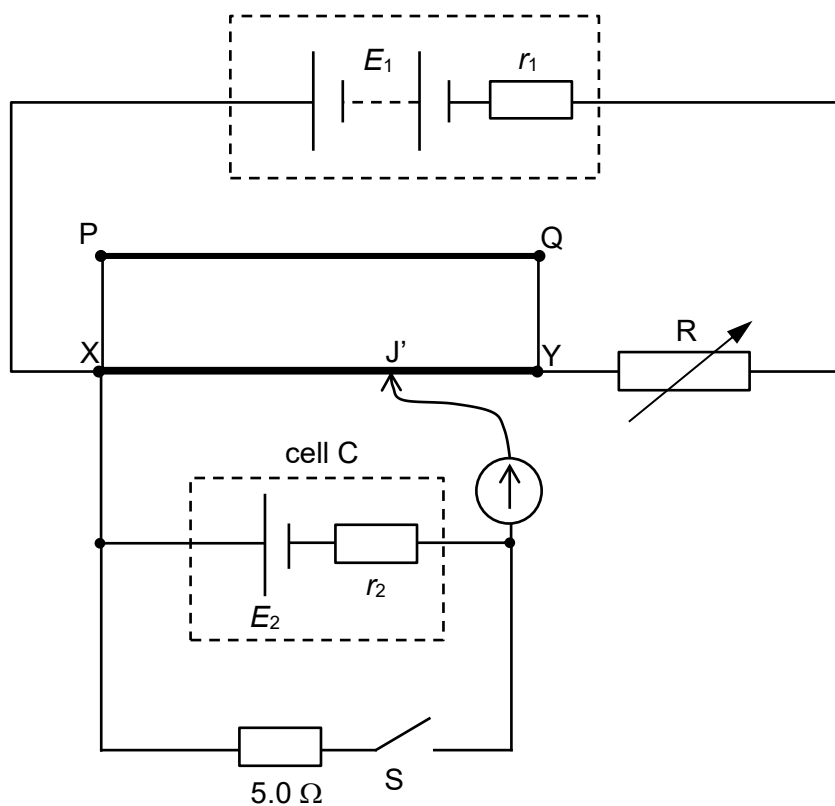

**Fig. 4.4**

State and explain if XJ' is smaller or larger than 0.75 m.

.....

.....

.....

.....

.....

..... [2]