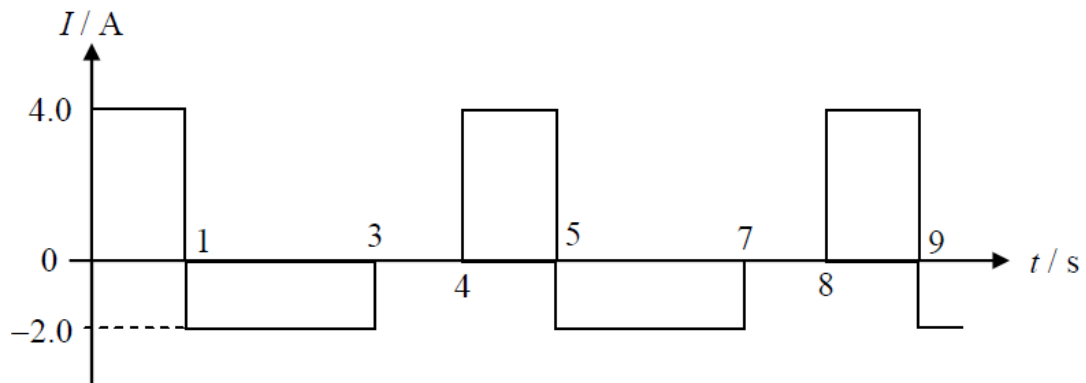


- 27 An alternating current with a rectangular waveform flows through a $11\ \Omega$ resistor.



What is the average power dissipated by the resistor?

- A** 0 W **B** 44 W **C** 66 W **D** 88 W

