

- 5 (a) A resistor of resistance  $R$  consists of a thin layer of copper deposited uniformly on the surface of an iron wire of radius of 0.60 mm and length 3.0 m as shown in Fig. 5.1. The thickness of the copper is  $1.78 \times 10^{-5}$  m.

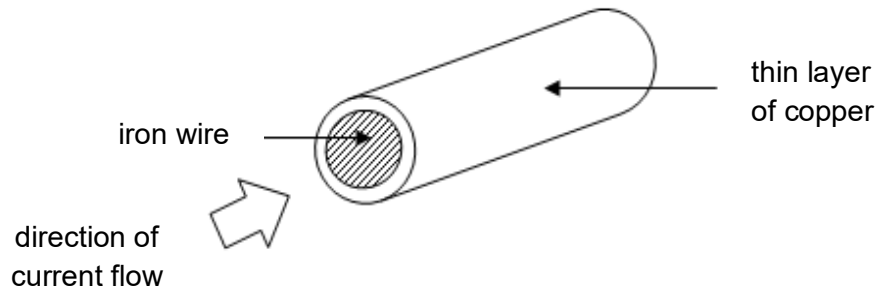


Fig. 5.1

- (i) The resistivity of iron and copper are  $8.90 \times 10^{-8} \Omega \text{ m}$  and  $1.60 \times 10^{-8} \Omega \text{ m}$  respectively.

If the resistance of iron wire is  $0.236 \Omega$ , show that  $R$  is  $0.18 \Omega$ .

[2]

- (ii) Explain how  $R$  changes after the current passes through it for a period of time.

.....  
 .....

.....

- (b) A 50 Hz 240 V alternating sinusoidal voltage is applied across the primary coil of a **step-down** transformer as shown in Fig. 5.2. A diode acting as a rectifier is placed in series with the resistor in (a) and the secondary coil.

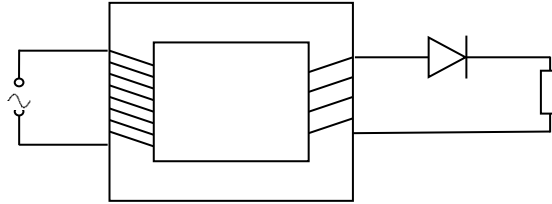



Fig. 5.2

The ratio  $\frac{\text{number of turns in primary coil}}{\text{number of turns in secondary coil}}$  is 10.

- (i) Determine the maximum output voltage from the transformer.

maximum output voltage = ..... V [2]

- (ii) On Fig. 5.3, sketch the variation with time the output power of the resistor. Label your graph clearly.

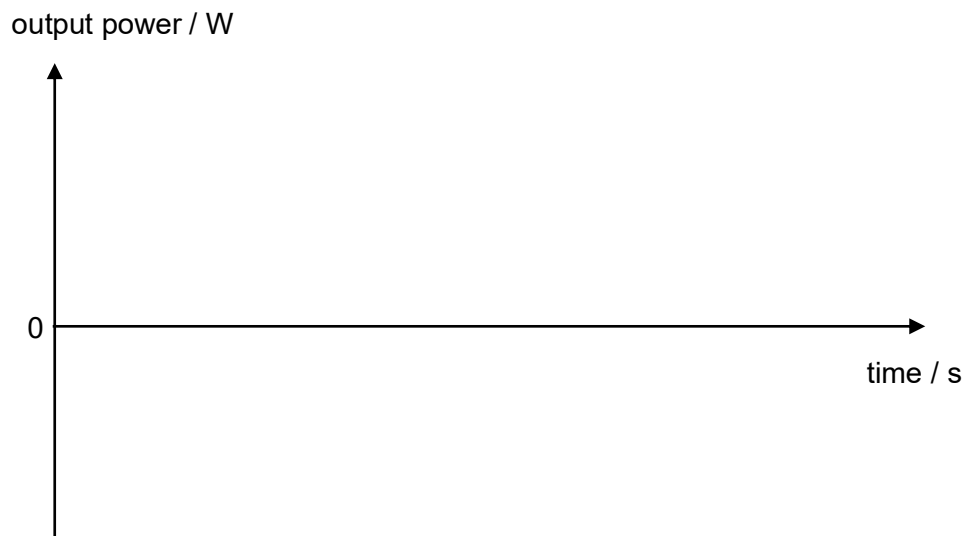


**Fig. 5.3**

[2]

- (iii) Hence, or otherwise, calculate the mean power generated by the resistor. Show your working clearly.

mean power = ..... W [3]

- (c) In a new electrical circuit as shown in Fig. 5.4, a direct current voltage of 24 V is connected across the resistor in (a). A diode is placed in series with the resistor.

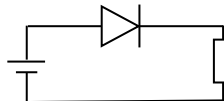

**Fig. 5.4**

Explain if there is any change to the mean power generated by the resistor as compared to your answer in (b)(iii).

.....  
...

..... [1]  
...

