

- 4 (a) The variation with potential difference (p.d.)  $V$  of current  $I$  of a semi-conductor diode is shown in Fig. 4.1.

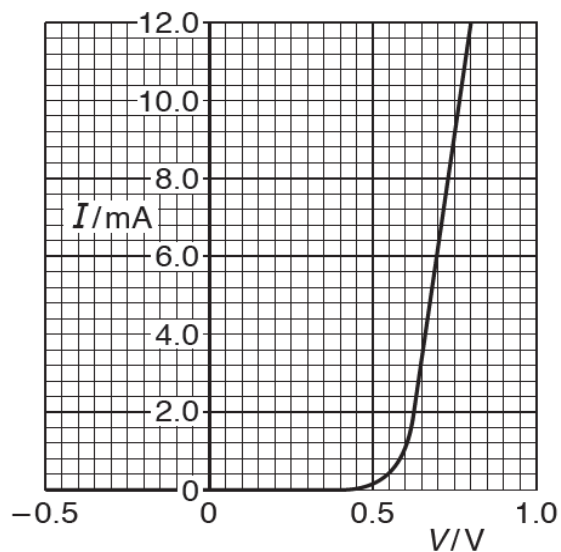


Fig. 4.1


- (i) Use Fig. 4.1 to describe the variation of the resistance of the diode between  $V = -0.5 \text{ V}$  and  $V = 0.8 \text{ V}$ .

.....  
 .....  
 .....  
 ..... [2]

- (ii) Determine the resistance of the diode at the instant when  $I = 0.4 \text{ mA}$ .

resistance = .....  $\Omega$  [2]


- (b) On Fig. 4.2, sketch the variation with p.d.  $V$  of current  $I$  for a filament lamp. Numerical values are not required.

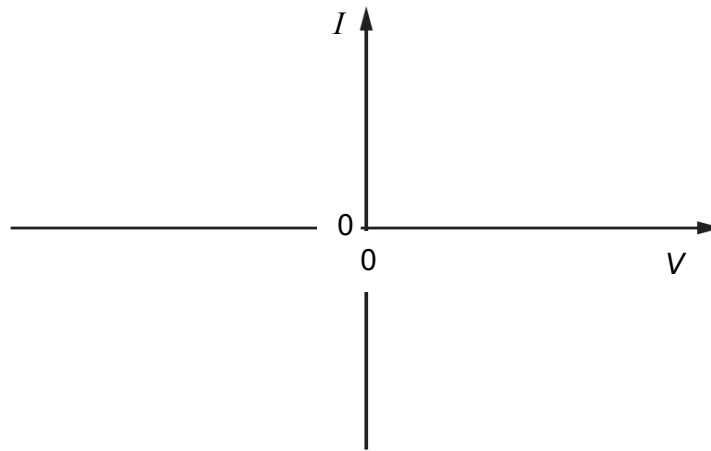

**Fig. 4.2**

[1]

- (c) Fig. 4.3 shows a power supply of electromotive force (e.m.f.) of 12 V and internal resistance  $0.50 \, \Omega$  connected to a filament lamp, a variable resistor and a switch.

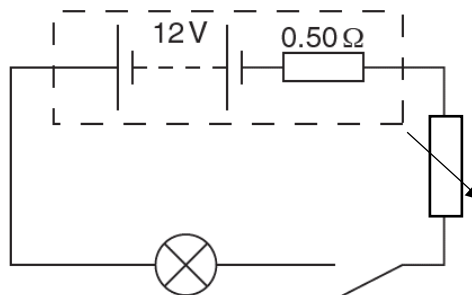

**Fig. 4.3**

- (i) The switch is closed. The filament lamp is rated at 20 W when the p.d. across it is 10 V. Calculate the resistance of the lamp.

resistance = .....  $\Omega$  [2]

- (ii) The variable resistor is adjusted to  $2.0\ \Omega$  and the p.d. across the lamp is now measured to be  $2.0\ \text{V}$ . Calculate the resistance of the lamp.

resistance = .....  $\Omega$  [2]

- (d) Explain how the two values of resistance calculated in (c) provide evidence for the shape of the sketch you have drawn in (b).

.....  
..... [1]



