

- 5 (a) A d.c. supply is connected across a variable resistor. The resistance of the variable resistor is changed. Fig. 5.1 shows the variation of the power  $P$  dissipated in the resistance  $R$  of the variable resistor.

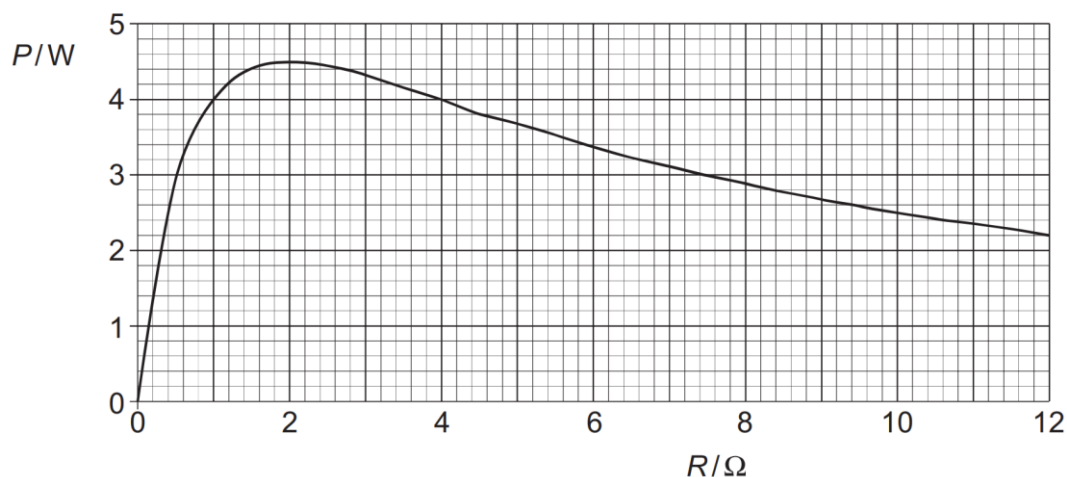


Fig. 5.1

- (i) Use Fig. 5.1 to determine the potential difference across the variable resistor when it dissipates maximum power.

potential difference = ..... V [2]

- (ii) Explain why your answer in (i) is not equal to the e.m.f. of the supply.

.....  
 .....  
 .....[1]

- (b) Fig. 5.2 shows a circuit. The battery has negligible internal resistance.

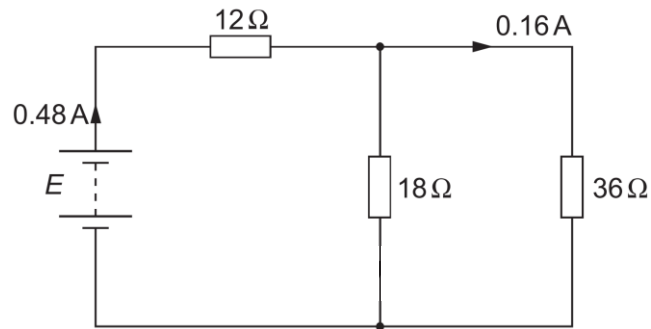


Fig. 5.2

- (i) Determine the number of electrons passing through the battery in a time of 150 s.

number = ..... [1]

- (ii) Determine the e.m.f.  $E$  of the battery.

e.m.f. = ..... V [2]