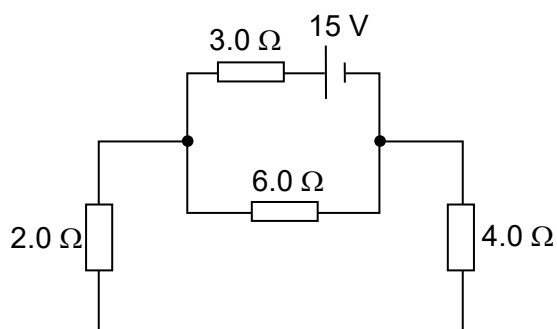


- 24** The diagram shows four resistors connected to a 15 V battery of negligible internal resistance.



What is the potential difference across the 6.0 Ω resistor?

- A** 2.5 V **B** 6.0 V **C** 7.5 V **D** 10 V

