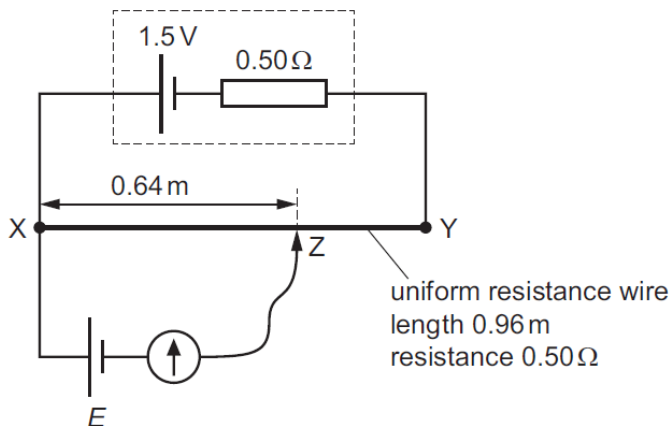


- 22 A potentiometer circuit is used to determine the electromotive force (e.m.f.)  $E$  of a cell. The circuit includes a second cell of e.m.f.  $1.5\text{ V}$  and internal resistance  $0.50\ \Omega$  that is connected to a uniform resistance wire  $XY$ , as shown.



The resistance wire  $XY$  has a length of  $0.96\text{ m}$  and a resistance of  $0.50\ \Omega$ .

The movable connection  $Z$  is moved along wire  $XY$ . The galvanometer reading is zero when length  $XZ$  is  $0.64\text{ m}$ .

What is the value of e.m.f.  $E$ ?

- A**  $0.50\text{ V}$                       **B**  $0.75\text{ V}$                       **C**  $1.0\text{ V}$                       **D**  $1.1\text{ V}$

- 23 The magnetic flux pattern formed in a region of space is shown