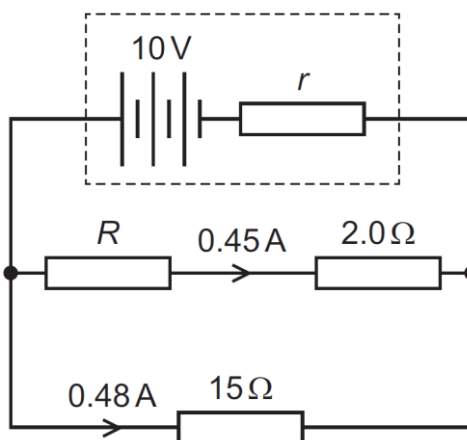


- 24** A battery of electromotive force (e.m.f.) 10 V and internal resistance r is connected to three resistors of resistances R , $2.0\ \Omega$ and $15\ \Omega$, as shown. A current of 0.45 A is in the resistor of resistance $2.0\ \Omega$ and a current of 0.48 A is in the resistor of resistance $15\ \Omega$.



What are the values of r and R ?

	r/Ω	R/Ω
A	3.0	14
B	3.0	20
C	5.8	14
D	5.8	20