

26

When a sinusoidal alternating current of peak value I_0 passes through a resistor of resistance R , the mean power dissipated in the resistor is P .

When another sinusoidal alternating current passes through the same resistor of resistance R , the mean power dissipated in the resistor is $4P$.

What is the root-mean-square value of this current?

|

A

$$\frac{I_0}{\sqrt{2}}$$

B

$$I_0$$

C

$$\sqrt{2}I_0$$

D

$$2I_0$$