

- 7 (a) A sinusoidal alternating current source is connected to a diode and a resistor as shown in Fig. 7.1 below.

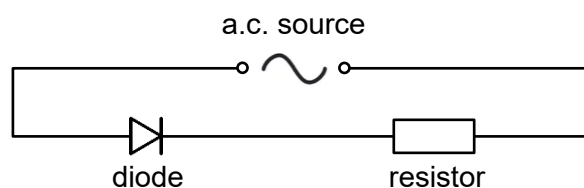


Fig. 7.1

The variation with time of the potential difference in the diode is shown in Fig. 7.2 below.

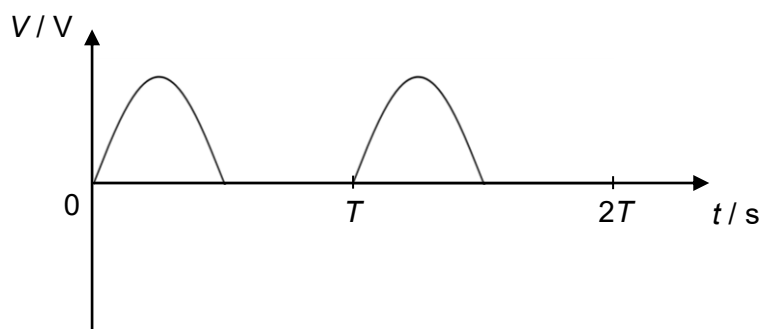


Fig. 7.2

- (i) On Fig. 7.3, sketch the variation with time of the potential difference across the resistor.

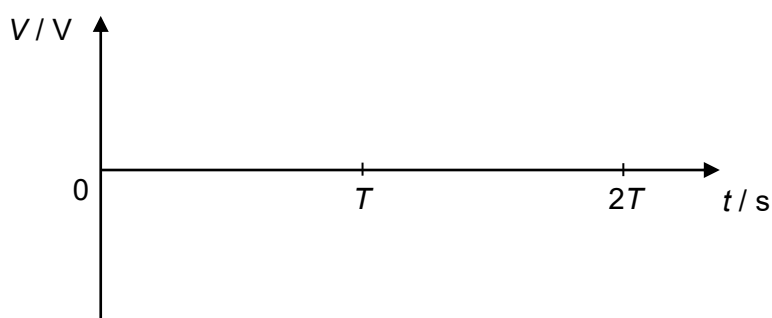


Fig. 7.3

[1]

- (ii) On Fig. 7.4, sketch the variation with time of the power in the resistor.

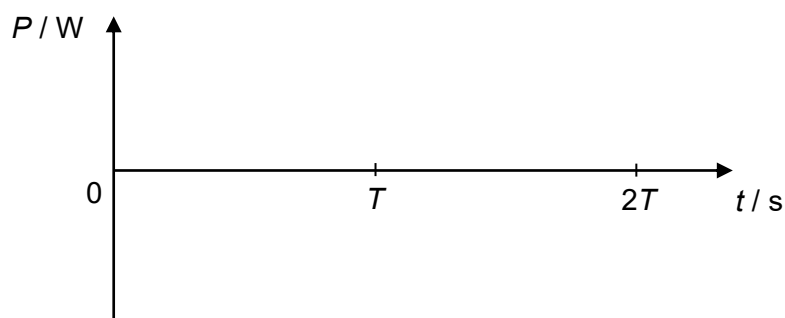


Fig. 7.4

[1]

- (iii) Given that the resistance of the resistor is $2.0\ \Omega$, and that the peak voltage in it is 5.0 V , calculate the average power dissipated.

average power = W [2]

- (b) Fig. 7.5 shows an ideal iron-cored transformer. The ratio of the secondary turns to the primary turns is 1:20.

A 230 V alternating current supply is connected to a primary coil and a $7.0\ \Omega$ resistor is connected to the secondary coil.

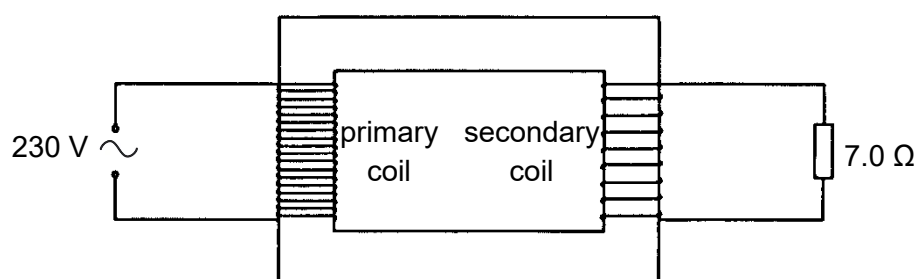


Fig. 7.5

- (i) Explain how an alternating current in the primary coil induces an electromotive force in the secondary coil.

.....

 [2]

- (ii) Determine the current in the primary coil.

current = A [2]