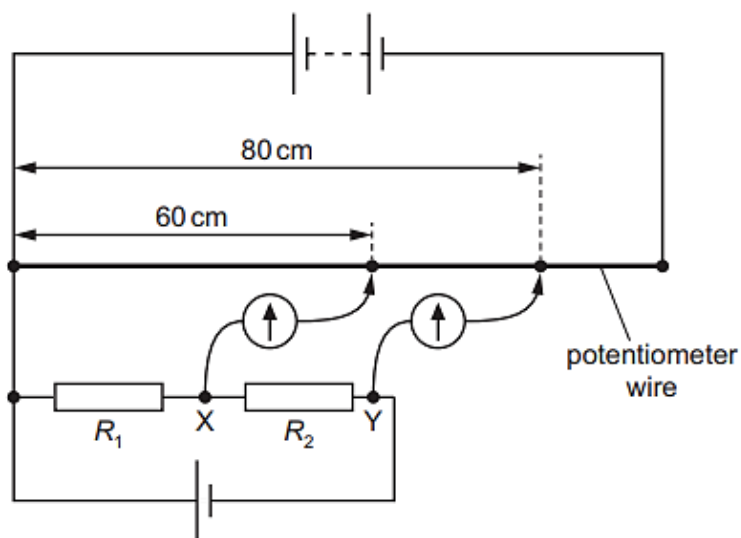


- 22 Potential differences across two resistors of resistances R_1 and R_2 are compared using a one metre long potentiometer wire of uniform resistance in the electrical circuit shown.



One galvanometer is connected from point X to the 60 cm mark. Another galvanometer is connected from point Y to the 80 cm mark. Both galvanometers read zero.

What is the ratio of $\frac{R_2}{R_1}$?

- A** 0.33 **B** 0.75 **C** 3.0 **D** 1.3