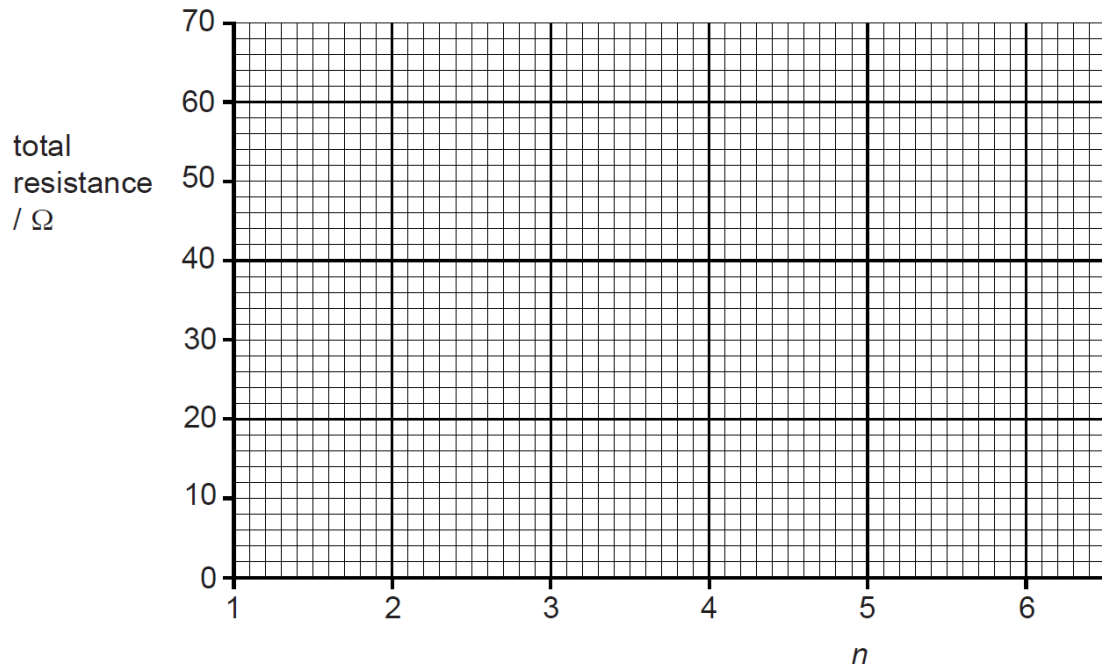


- 6 (a) (i) 1. Give an expression for the total resistance of n resistors, each of resistance $10\ \Omega$, connected in **series**, where n is the number of resistors.

resistance = Ω [1]

2. On Fig. 6.1, plot a graph showing the values of the total resistance for $n = 1, 2, 3, 4, 5$ and 6 . Label the line S.



[2]

Fig. 6.1

- (ii) 1. Give an expression for the total resistance of n resistors, each of resistance $10\ \Omega$, connected in **parallel**, where n is the number of resistors.

resistance = Ω [1]

2. On Fig. 6.1, plot a graph showing the values of the total resistance for $n = 1, 2, 3, 4, 5$ and 6 . Label the line P.

[2]

- (b) (i) Fig. 6.2 shows a network of 16 resistors, each of resistance $10\ \Omega$ connected in four parallel lines of four resistors in series.

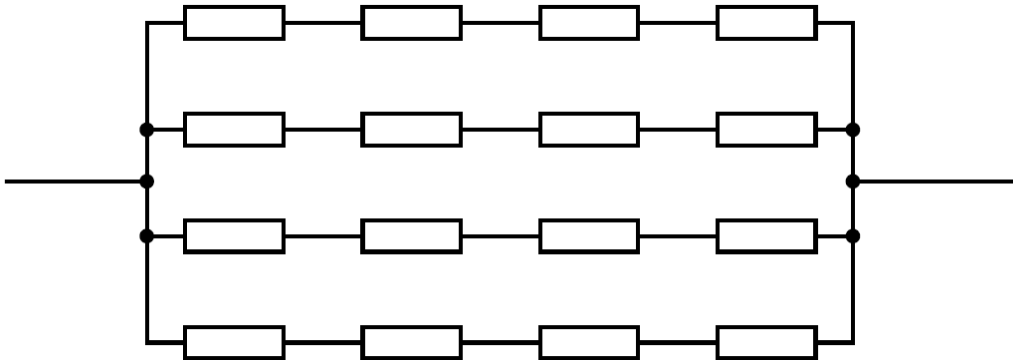


Fig. 6.2

Calculate the total resistance of the network.

total resistance = Ω [1]

- (ii) State the total resistance of a network of n parallel lines of n resistors in series where every resistor has a resistance of $10\ \Omega$.

resistance = Ω [1]

- (iii) Explain one practical advantage of using many individual resistors in this way, rather than using a single resistor.

.....

.....

[1]

[Total: 9]