

- 5 A battery of e.m.f. 4.8 V and negligible internal resistance is connected to four resistors as shown in Fig. 5.1.

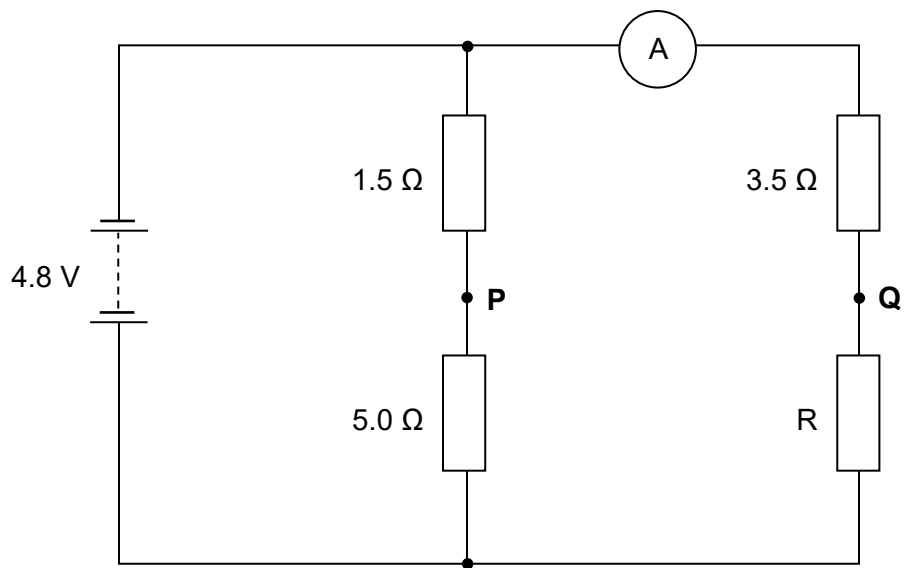


Fig. 5.1

The ammeter reading is 0.80 A.

- (a) Determine the resistance of resistor R.

resistance of R = Ω [2]

(b) Resistor R is a metallic ohmic resistor.

- (i) On Fig. 5.2, draw the I - V characteristic graph of resistor R at constant temperature.
[1]

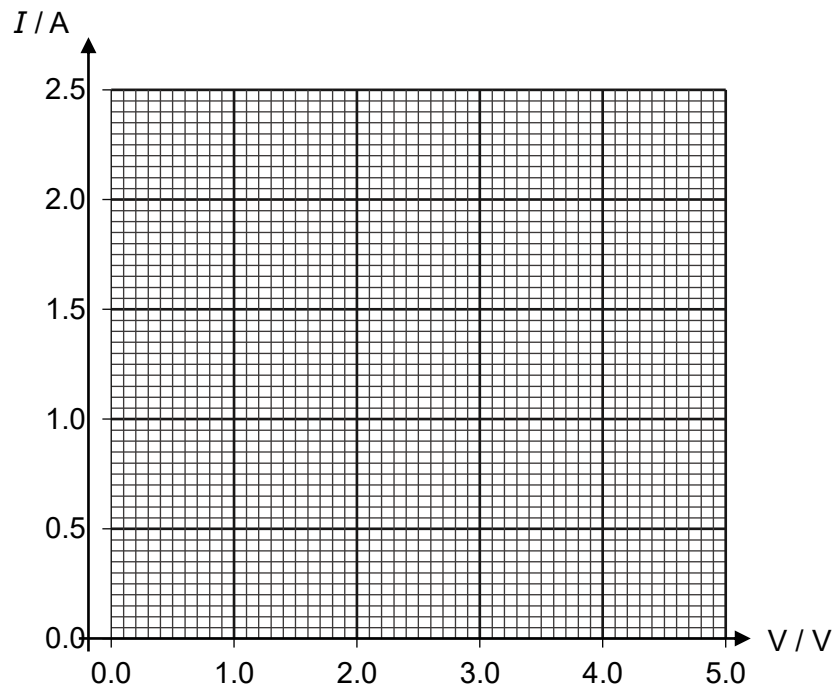


Fig. 5.2

- (ii) With reference to your graph, explain the relationship between the drift velocity and the potential difference across the ohmic resistor of uniform cross-sectional area.

.....
.....
.....
.....
.....[2]

- (iii) Calculate the electrical energy supplied by the battery in one hour.

electrical energy = J [3]

- (iv) Points **P** and **Q** are points in the circuit as shown in Fig. 5.1. Determine the potential of **Q** with respect to **P**.

potential = V [2]

