

- 4 (a) A battery of electromotive force (e.m.f.)  $9.0\text{ V}$  and internal resistance  $r$  is connected to two resistors S and T, as shown in Fig. 4.1.

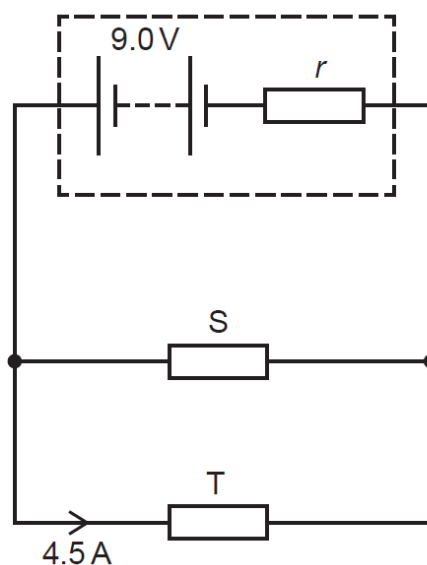


Fig 4.1

A total charge of  $650\text{ C}$  moves through resistor S in a time interval of  $540\text{ s}$ . During this time resistor S dissipates  $4800\text{ J}$  of energy. The current in resistor T is  $4.5\text{ A}$ . Assume that the e.m.f. of the battery remains constant.

Calculate:

- (i) the current in resistor S

current = .....A [1]

- (ii) the internal resistance  $r$  of the battery.

$$r = \dots\dots\dots \Omega \quad [3]$$

**[Turn over**

- (b)** A sinusoidal alternating voltage has a root-mean-square (r.m.s.) potential difference (p.d.) of 4.2 V and a frequency of 50 Hz.

- (i)** By reference to heating effect, explain what is meant by the root-mean-square (r.m.s.) value of an alternating current.


.....  
 .....  
 .....[1]

- (ii)** The alternating voltage is applied across a resistor of resistance 760  $\Omega$ .

Determine the maximum power dissipated by the resistor.

$$\text{maximum power dissipated} = \dots\dots\dots \text{ mW} \quad [2]$$

- (iii)** On Fig. 4.2, sketch the variation with time  $t$  of the power  $P$  transferred in the resistor. Include on your graph a time equal to two periods of the alternating potential difference.

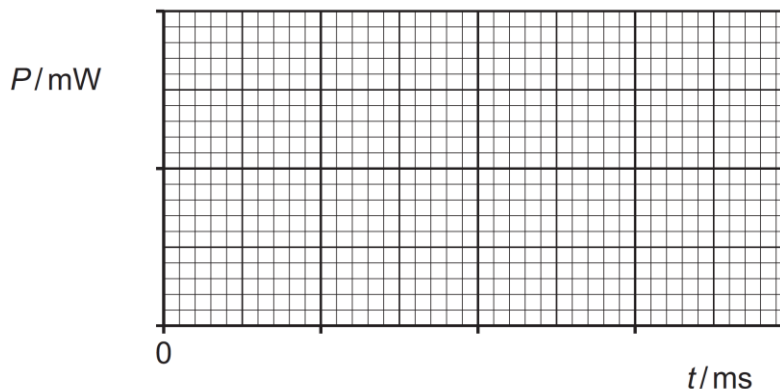

**Fig. 4.2**

[3]

[Total: 10]