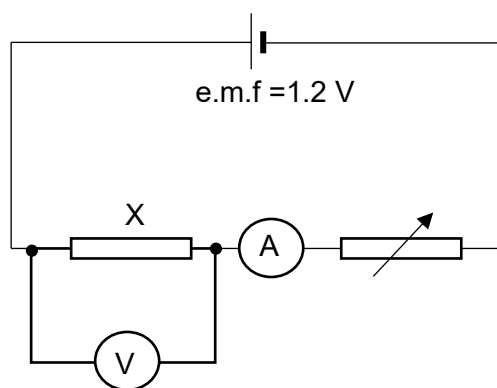


9(a) A metal wire X of length 6.0 cm and diameter 0.30 mm is made of a material with resistivity  $1.50 \times 10^{-6} \Omega \text{ m}$  at room temperature.

(i) Show that the resistance of X at room temperature is  $1.3 \Omega$ . [2]

(ii) The metal wire X is placed in a circuit in series with an ideal cell of e.m.f. of 1.2 V and a variable resistor. An ideal voltmeter is connected across X to measure its p.d.  $V$ , and an ideal ammeter is connected in series with X to measure its current  $I$ , as shown in Fig. 9.1:



**Fig. 9.1**

1. Distinguish between e.m.f. and p.d.

[2]

.....

.....

.....

2. As the current through X is increased, its temperature rises.  
Sketch an  $I - V$  characteristic graph for X. [1]

3. Explain how the graph in (ii)2. can be used to determine the resistance of X for a given value of  $V$ . [1]


.....

.....

4. The variable resistor is set to  $0.50 \Omega$ . Using the value of the resistance of X that you found in (i), calculate the fraction of the power delivered by the cell that is dissipated through X. [2]

Fraction = .....

- (b) A light bulb is placed in a circuit with a rheostat and an ideal voltmeter connected across it. The resistance of the rheostat can be varied from  $0 \Omega$  to  $10 \Omega$ . The combination is placed in series with an ideal cell of e.m.f.  $3.0 \text{ V}$  and a resistor S of  $0.60 \Omega$ , as shown in Fig. 9.2:

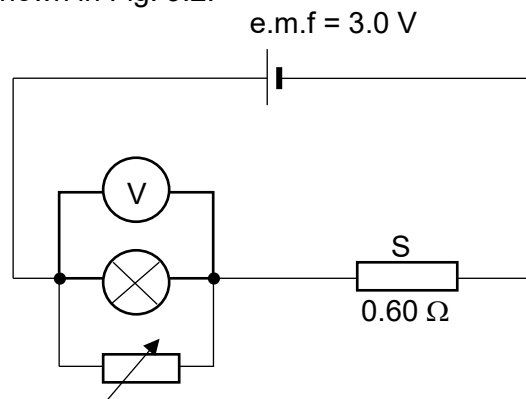

**Fig. 9.2**

- (i) Explain how the reading on the voltmeter will change as resistance of the rheostat is varied from minimum to maximum value. [3]

.....

.....

.....

.....

.....

- (ii) Explain the purpose of resistor S. [2]

.....

- (iii) When the rheostat is set to the maximum setting of  $10\ \Omega$ , the voltmeter reads 1.2 V.

1. Calculate the current delivered by the cell. [2]

Current = .....

2. Calculate the current flowing through the light bulb. [3]

Current = .....

3. A student suggests that the rheostat can act as a switch for the light bulb, since setting the resistance of the rheostat to  $0\ \Omega$  will cause the current in the light bulb to drop to  $0\ \text{A}$ . Explain why it is not practical to use the rheostat as a switch. [2]

.....

.....

.....

**End of paper**

**BLANK PAGE**