

- 26** A 240 V supply is connected to a step down transformer. The output of the transformer is connected to five 12 V, 24 W lamps connected in parallel.

Each lamp operates at normal brightness and the transformer is 100% efficient.

What is the current drawn from the supply?

A 0.10 A

B 0.50 A

C 2.0 A

D 10.0 A