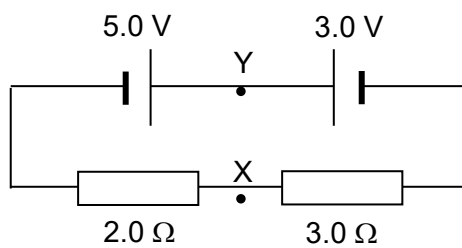


- 22** A circuit is connected as shown below. The internal resistance of each cell is negligible.



What is the potential difference between point X and point Y?

- A** 0.80 V **B** 1.2 V **C** 3.0 V **D** 4.2 V